

학번: _____ 이름: _____

Final Exam (2.5 hours)

For all multiple questions,

- ✓ Indicate your confidence level to the first decimal between 0 ~ 1 (0: wild guess ~ 1: very confident).
- ✓ -1 point if incorrect. Your score = point x confidence level
- ✓ e.g.) 2pts x 0.6 (confidence level) = 1.2pt e.g.) -1pt x 1 (confidence level) = -1 pt

1. Consider a device whose I-V characteristic is $V = K I^2$, where K is a constant. [4pts]

(a) Can you use superposition to analyze a circuit that has this device? [2pts]


(Yes, **No**) Confidence level: ()

(b) Can you use KCL or KVL to analyze this circuit? [2pts]

1) You can use KCL only. 2) You can use KVL only. **3) You can use both KCL and KVL.** 4) You cannot use KCL nor KVL.

Confidence level: ()

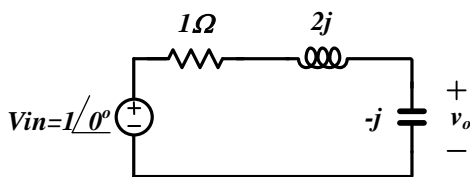2. Consider the circuit shown below where the input voltage (v_i) is $\sin(2t)$ which is represented in phasor as $1\angle 0^\circ$. [8pts]



(a) What is the output voltage, v_o ? Express your answer in complex numbers. [2pts]

Sol) $1\angle 0^\circ \times \frac{-j}{1+2j-j} = -\frac{1}{2} - \frac{1}{2}j$

(b) Suppose the input voltage is changed to $\cos(t)$, what is the output voltage, v_o ? Express your answer in complex numbers. [3pts]

Sol) 아래 세 경우 모두 정답 Answer is right in those 3 cases below,

Case1) $1\angle 0^\circ \times \frac{-2j}{1+j-2j} = 1 - 1j$

Case2) $1\angle 90^\circ \times \frac{-2j}{1+j-2j} = 1 + 1j$

Case3) 주파수가 바뀌었음으로 표현할 수 없음 (can't express it since w has changed)

부분점수) 아래와 같이 inductor와 capacitor 값을 변경한 것이 보일 경우: +1.5점

$$\frac{-j(\text{capacitor})}{1 + 2j(\text{inductor}) - j(\text{capacitor})} \rightarrow \frac{-2j(\text{capacitor})}{1 + j(\text{inductor}) - 2j(\text{capacitor})}$$

(c) Suppose the input voltage is changed $\sin(2t) + \cos(t)$. What is the output voltage, v_o ? Assume that your answer to (a) and (b) are $a+bj$ and $c+dj$, respectively. Express your answer in time domain. Use a, b, c, d to express your answer. [3pts]


Sol) $v_{o,1} = \sqrt{a^2 + b^2} \cdot \sin\left(2t + \tan^{-1}\frac{b}{a}\right), \quad v_{o,2} = \sqrt{c^2 + d^2} \cdot \cos\left(t + \tan^{-1}\frac{d}{c}\right)$

$$\therefore v_o = \sqrt{a^2 + b^2} \cdot \sin\left(2t + \tan^{-1}\frac{b}{a}\right) + \sqrt{c^2 + d^2} \cdot \cos\left(t + \tan^{-1}\frac{d}{c}\right)$$

부분점수 1) 답에 $\sqrt{a^2 + b^2}$ 또는 $\sqrt{c^2 + d^2}$ 가 존재할 경우: +0.5점 (if those terms exists, +0.5 points)

부분점수 2) 답에 $\sin\left(2t + \tan^{-1}\frac{b}{a}\right)$ 또는 $\cos\left(t + \tan^{-1}\frac{d}{c}\right)$ 가 존재할 경우: +0.5점

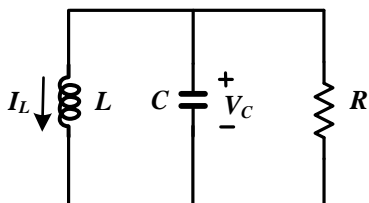3. Consider the below RLC circuit, where the initial conditions are $V_C(0) = 1\text{V}$, $I_L(0) = 0\text{A}$. [14pts]



(a) What kind of response does this circuit have when $R=12.5\Omega$, $L=4\text{H}$ and $C = 0.01\text{F}$? [2pts]

- 1) Overdamped 2) **Underdamped** 3) Critically damped Confidence level: ()

(b) What is the transient waveform of V_C for $t>0$? Please provide a mathematical expression. [3pts]



$$V_C(t) = e^{-4t}(\cos 3t - 4/3\sin 3t)$$


$$V_C(t) = e^{-A_1 t}(B_1 \cos C_1 t + B_2 \sin C_2 t)$$

부분점수: A_1, B_1, B_2, C_1, C_2 틀릴 경우 각 경우 마다 -0.5 점

(c) Suppose it is possible to use negative resistance. By using a negative resistance, please modify the circuit so that it produces a sustained oscillation with finite amplitude. [3pts]

두 경우를 제외 하고 0 점

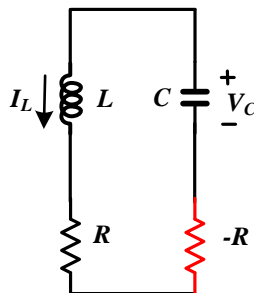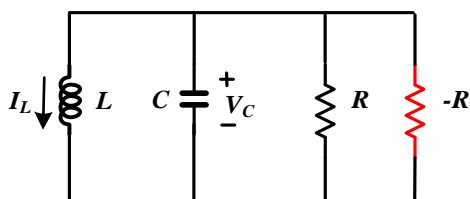


(d) Suppose the resistor is replaced by a device that has an I-V characteristic of $V = (100I)^3$. ($I \downarrow$  $V = (100I)^3$) What kind of response do you expect to see? [3pts]

- 1) Overdamped 2) Underdamped 3) Critically damped 4) First-order system 5) **Underdamped or critically to overdamped**
6) Overdamped to critically or underdamped. 7) None of the above. Confidence level: ()

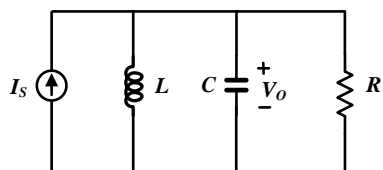(e) Suppose a current source is added as shown below, where $I_s = I_0 \sin\left(\frac{t}{\sqrt{LC}}\right)$. [3pts]

What is the amplitude of the steady-state output voltage? (Definition of amplitude: $A_0 \sin(t)$ has amplitude of A_0 .)




$$V_o = I_s \times R = I_0 R \sin\left(\frac{1}{\sqrt{LC}} \cdot t\right), \text{ at } \omega = \sqrt{\frac{1}{LC}}$$

$$A_o = I_o \times R$$

$$V_o = I_s \times Z = I_s (j\omega L \parallel \frac{1}{j\omega C} \parallel R)$$

부분 점수: 1) Impedance Z 를 적어만 놓은 학생 0.5 점(+0.5 points for those who only wrote impedance Z right)

2) 공진 주파수에서 L-C 에 의한 Impedance 가 무한대임을 인지하였으나, $V = I/R$ 로 정답을 작성한 학생 1 점 (recognized that LC impedance is infinite, but wrote the answer as $V = I/R$, +1 point)

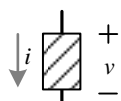4. Consider a two terminal device  whose I-V characteristic is $v(t) = K \frac{d^2 i(t)}{dt^2}$, where K is a constant. [17pts]

(a) What is the total phase shift due to this device for a sinusoid voltage or current? Express your answer using K. [2pts]

Sol) $K \geq 0$: 180° or -180° or π or $-\pi$ & $K < 0$: 0

(b) Find a frequency domain representation (e.g. capacitor is $1/j\omega C$) of this device for the case when input voltage is $\sin(10t)$. Express your answer using K. [2pts]

Sol) $-100K$: pt

(Partial score) $100K$: 1pt -100 : 1pt 100 : 0pt

(c) Find the I-V characteristic of this device in s-domain (Laplace transform) when all initial conditions are zero. (e.g. express $V(s)$ using $I(s)$, s, and K) [2pts]

Sol) $V(s) = Ks^2 I(s) - sf(0^-) - f'(0^-) = Ks^2 I(s)$ \because all initial conditions are zero

or $Z(s) = V(s)/I(s) = Ks^2$


(d) Repeat (c) when initial conditions are not zero. Express your answer using K, $I_{p0} = di/dt|_{t=0}$ and $I_0 = i(0)$ [3pts]

Sol) $V(s) = Ks^2 I(s) - KsI_0 - KI_{p0}$


(Partial score) 부호 틀릴 시 개당 -1pt

1pt per a term : ex1) $V(s) = Ks^2 I(s) - KI_{p0}$: 2pt ex2) $V(s) = Ks^2 I(s) + KsI_0$: 1pt

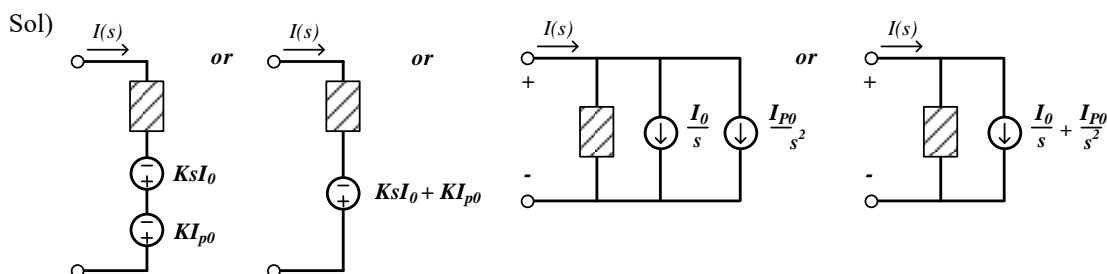(e) Draw the equivalent circuit model for (d). [3pts]



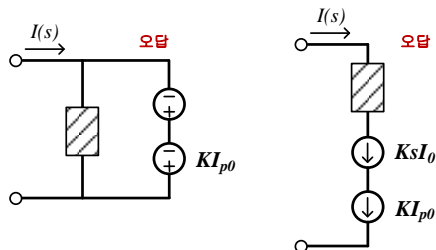
(Partial score) 부호 or voltage source 방향 틀릴 시 개당 -1pt




(f) What are possible waveforms of the below circuit in v_o ? Choose all that applies. Assume zero initial condition. [3pts]

Sol) $V_O(s) = \frac{Ks}{Ks^2 + R}$

$v(t) = \cos(\sqrt{\frac{R}{K}}t)$

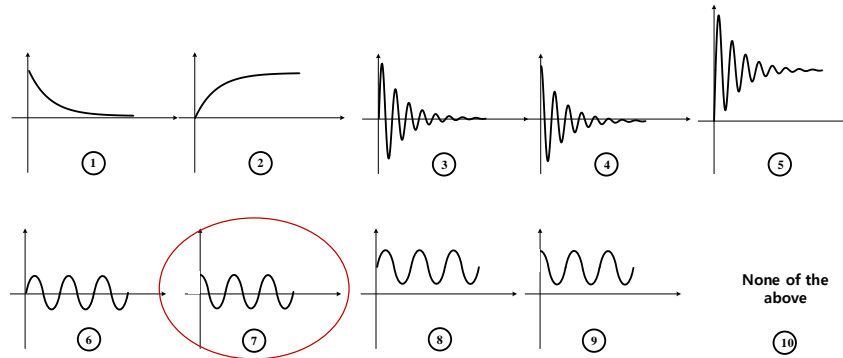

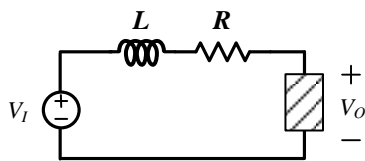
(g) Consider the circuit shown below. What kind of filtering function does the above circuit provide from V_I to V_O ? [2pts]



- 1) low-pass 2) band-pass **3) high-pass** 4) band-stop

Confidence level ()

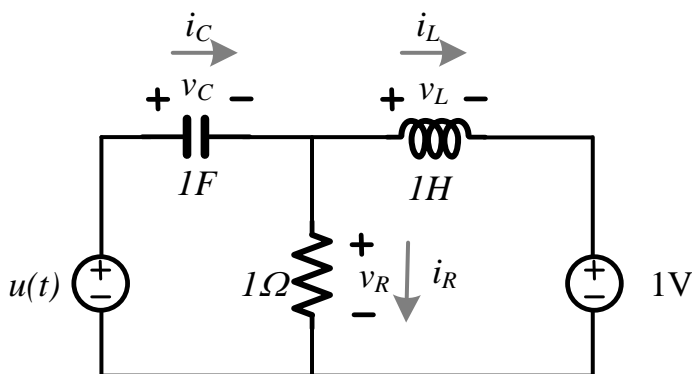5. Please fill in the below table. RLC circuits. Only the underlined cells will be graded. [13pts]



at $t=0^-$

i_R	<u>1 [A]</u>	v_R	1 [V]
i_C	<u>0 [A]</u>	v_C	-1 [V]
i_L	<u>-1 [A]</u>	v_L	0 [V]

at $t=0^+$


i_R	<u>2 [A]</u>	v_R	2 [V]
i_C	<u>1 [A]</u>	v_C	<u>-1 [V]</u>
i_L	<u>-1 [A]</u>	v_L	<u>1 [V]</u>

at $t=0^+$


di_R/dt	<u>-1 [A/s]</u>	dv_R/dt	-1 [V/s]
di_C/dt	<u>0 [A/s]</u>	dv_C/dt	<u>1 [V/s]</u>
di_L/dt	<u>1 [A/s]</u>	dv_L/dt	<u>-1 [V/s]</u>

Ans) each cell is worth 1point (Correct: 1pt, Incorrect: 0pt). No deduction for missing units.

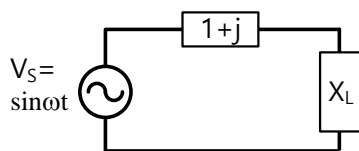6. [AC power] Consider the circuits shown below. [10pts]



Problem (a)

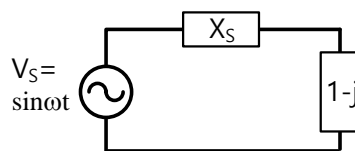

Problem (b)

(a) In the left circuit (a), find X_L that will result in maximum power transfer to the load X_L . [2pts]

Ans) $1-j$

(b) In the right circuit (b), find X_S that will result in maximum power transfer to the load $1-j$. [2pts]

Ans) j

(c) What is the power factor (PF) for your answer to (a)? [2pts]

Ans) 1

(d) Suppose the input voltage V_S is changed to $\sin(\omega t + 90^\circ)$ in Fig. (a). [2pts]

Does your answer in (a) still result in maximum power transfer? (Yes, No) Confidence level () [1pts]


How about PF? (Increases, Decreases, stays the same) Confidence level () [1pts]

(e) Suppose there is another current source $I_S = \cos(\omega t)$ as shown below [2pts]


Does your answer in (a) still result in maximum power transfer for both V_S and I_S ?

(Yes, No) Confidence level () [1pts]

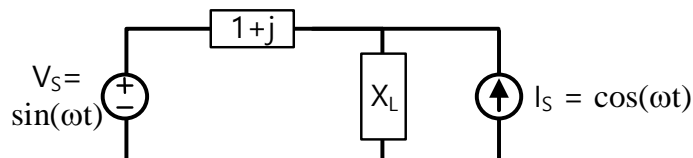How about PF for V_S and I_S ? (Increases, Decreases, stays the same) Confidence level () [1pts]



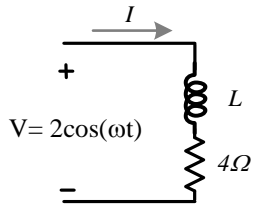7. Consider the circuit shown below. [11pts]



(a) What is the apparent power? Express your answer using ω and L . [2pts]

Ans) $\frac{1}{2} \frac{4}{\sqrt{\omega^2 L^2 + 16}}$

+1pts if 1/2 is omitted

+0.5pts if only denominator is correct

(b) Suppose the power factor (PF) is 0.8. What is L when $\omega=3$? [2pts]

Ans) 1H


Correct even if there is no unit

(c) Consider the circuit shown below. What circuit element should X be and what is its value so that $PF = 1$. [5pts]

X is a (resistor, inductor, capacitor) (1pt) Confidence level ()

Current through X represented in complex number is $-0.5j$ (2pt)

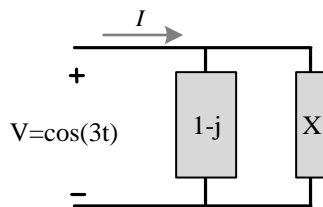
The value of X is $2/3 \Omega/H/F$ (2pt).



(d) In Korea, does your electric bill increase when you use devices of power factor less than 1 ? [2pts]

(Yes, No) Confidence level ()

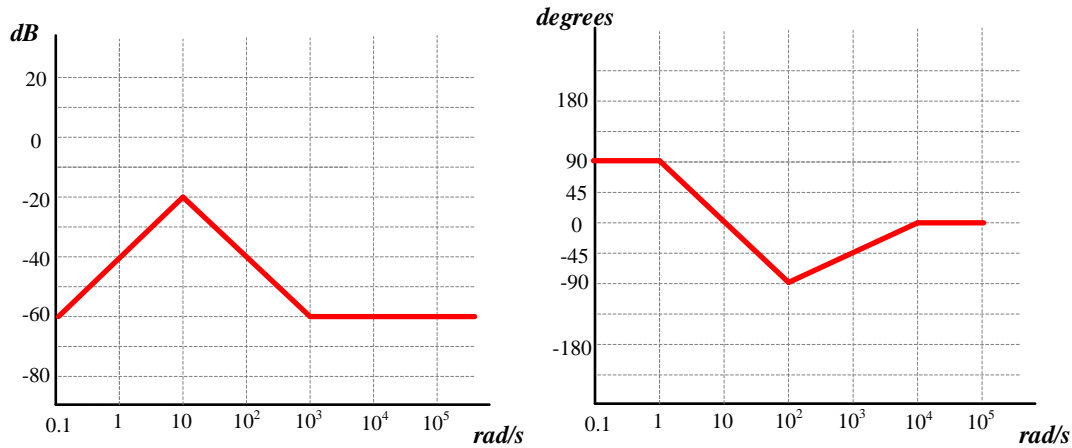8. Draw the bode plot of the below transfer function. $H(s) = \frac{s \cdot (1 + s/1000)}{100 \cdot (1 + s/10)^2}$ [8pts]



채점기준(dB)

Right answer: 4점

If suited in those cases + x points per each cases (Overall 3 points for all right cases)

0.1~10 range + 20dB/dec: + 0.5점

10~1000 range: -20dB/dec: + 0.5점

1000~ to the end: 0dB/dec: + 0.5점

At 0.1rad/s crosses -60dB point: + 0.5점

At 10rad/s crosses -20dB point: + 0.5점

At 1000rad/s crosses -60dB point: + 0.5점

채점기준(dB)

Right answer: 4점

If suited in those cases + x points per each cases (Overall 3.5 points for all right cases)

0.1~1 range: + 0°/dec: + 0.5점

10~100 range: -90°/dec: + 0.5점

100~10000 range: + 45°/dec: + 0.5점



10000~ to the end: 0/dec: + 0.5점

At 0.1rad/s crosses + 90° point: + 0.5점

At 100rad/s crosses -90° point: + 0.5점

At the last frequency crosses + 0° point: + 0.5점

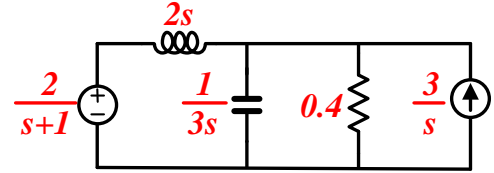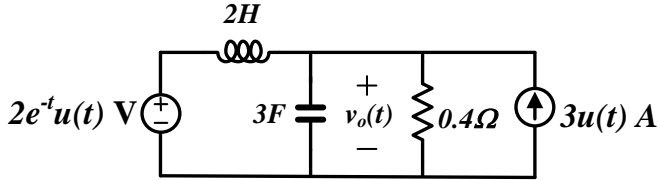9. Consider the circuit shown below. [6pts]



(a) Find the values of the circuit shown above in s-domain by using Laplace transform. Assume all initial conditions are zero. [2pts]

Sol) 저항은 점수 없음. 나머지 0.5점씩 (No points for Resistance. Others are 0.5 points each)

(b) Express V_O in s-domain. [2pts]

Sol) (a)가 틀린 경우, (b) 무조건 틀림 (If (a) is wrong, (b) is also wrong)

Case1)

$$\frac{\frac{2}{s+1} - v_o}{2s} + \frac{3}{s} = \frac{v_o}{1/3s} + \frac{v_o}{0.4}$$

$$\frac{2}{s+1} + 6 = (6s^2 + 5s + 1) \cdot v_o \rightarrow v_o = \frac{6s+8}{s+1} \cdot \frac{1}{6s^2 + 5s + 1} = \frac{6s+8}{s+1} \cdot \frac{1}{(2s+1)(3s+1)}$$

Case2)

$$v_o = \frac{2}{s+1} \cdot \frac{\frac{1}{3s} \parallel 0.4}{\left(2s + \frac{1}{3s} \parallel 0.4\right)} + \frac{3}{s} \cdot \left(2s \parallel \frac{1}{3s} \parallel 0.4\right)$$

$$v_o = \frac{2}{s+1} \cdot \frac{2}{12s^2 + 10s + 2} + \frac{3}{s} \cdot \frac{4s}{12s^2 + 10s + 2} = \left(\frac{4}{s+1} + 12\right) \cdot \frac{1}{12s^2 + 10s + 2} = \frac{6s+8}{s+1} \cdot \frac{1}{(2s+1)(3s+1)}$$

$$\therefore v_o = \frac{6s+8}{(s+1)(2s+1)(3s+1)} = \frac{1}{s+1} - \frac{20}{2s+1} + \frac{27}{3s+1} = \frac{1}{s+1} - \frac{10}{s+1/2} + \frac{9}{s+1/3}$$

부분점수 1) 분모에 $(2s+1)$ 또는 $(s+1/2)$ 가 존재할 경우: +0.5점 (if those term exist in Denominator, +0.5 points)

부분점수 2) 분모에 $(3s+1)$ 또는 $(s+1/3)$ 가 존재할 경우: +0.5점

부분점수 3) 계산식 전개 과정 중 계산 틀릴 경우: 감점 없음. (Calculation mistake: no points deducted)

(c) Find the inverse Laplace transform of $\frac{2s^2 + 3s + 2}{s^3 + 2s^2 + 2s}$ [2pts]

Sol)

$$\frac{2s^2 + 3s + 2}{s(s^2 + 2s + 2)} = \frac{A}{s} + \frac{B}{s^2 + 2s + 2} = \frac{1}{s} + \frac{s+1}{s^2 + 2s + 2} = \frac{1}{s} + \frac{s+1}{(s+1)^2 + 1}$$

$$\therefore \text{Laplace transform of } \frac{1}{s} + \frac{s+1}{(s+1)^2 + 1} = (1 + e^{-t} \cos t)u(t)$$

부분점수 1) $u(t)$ 없는 경우: -0.5점 (no $u(t)$: -0.5 points)

부분점수 2) \cos 을 \sin 으로 적은 경우: -0.5점 (wrote \sin in place of \cos : -0.5 points)



부분점수 3) \cos 없는 경우: -1.0점 (didn't write \cos term: -1point)

부분점수 4) a, b, c, d가 틀릴 경우 각 경우 마다: -0.5점 (-0.5 points for each a, b, c, d)

$$(a + be^{-ct} \cos dt)u(t)$$

부분점수 5) 그외의 경우: 점수 0점 (other cases: 0 point)

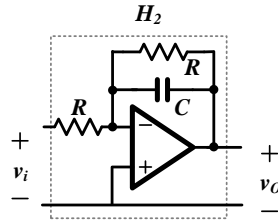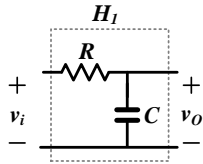10. Consider the circuit shown below. [9pts]



(a) What is the transfer function $H_1=V_o(s)/V_i(s)$? [2pts]

Sol)

$$H_1(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + sCR}$$

채점기준

2점: $\frac{1}{sC}, \frac{1}{1 + sCR}, \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}, \frac{1}{1 + j\omega CR}$ (전개 하지 않아도 됨, no need for expansion)

0.5점: $\frac{1}{\omega C}, \frac{1}{1 + \omega CR}$ ($s = j\omega$ 가 아니라 $s = \omega$ 로 쓴 경우, wrote s as w instead of jw)

이외의 경우 모두 0점 (otherwise, 0 points)

(b) What is the transfer function $H_2=V_o(s)/V_i(s)$? [2pts]

Sol)

$$-\frac{V_i}{R} - \frac{V_o}{R \parallel \frac{1}{sC}} = 0$$

$$H_2(s) = \frac{V_o(s)}{V_i(s)} = -\frac{R \parallel \frac{1}{sC}}{R} = -\frac{1}{R} \times \frac{1}{\frac{1}{R} + sC} = -\frac{1}{R} \times \frac{R}{1 + sCR} = -\frac{1}{1 + sCR}$$

채점기준



2점: $-\frac{R \parallel \frac{1}{sC}}{R}, -\frac{1}{1 + sCR}, -\frac{R \parallel \frac{1}{j\omega C}}{R}, -\frac{1}{1 + j\omega CR}$ (전개 하지 않아도 됨, no need for expansion)

1.5점: 부호가 틀린 경우

0.5점: $-\frac{R \parallel \frac{1}{\omega C}}{R}, -\frac{1}{1 + \omega CR}$ ($s = j\omega$ 가 아니라 $s = \omega$ 로 쓴 경우, wrote s as w instead of jw)

이외의 경우 모두 0점 (otherwise, 0 points)

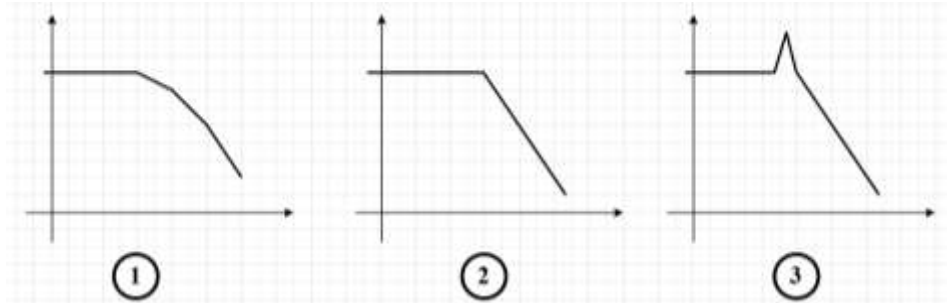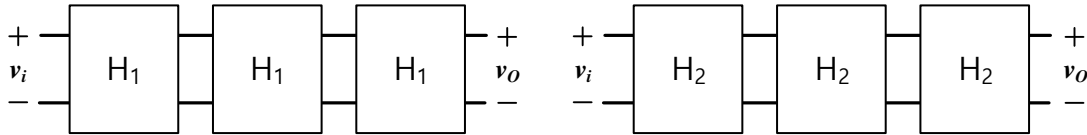
- (c) Suppose a sharp roll-off low-pass filter is desired. One student designed it using cascaded H_1 while another used cascaded H_2 . Choose the correct magnitude Bode plots of cascaded H_1 and cascaded H_2 . [3pts]



Cascaded H_1 : ①, ②, ③ Confidence level () [1.5pt]

Cascaded H_2 : ①, ②, ③ Confidence level () [1.5pt]

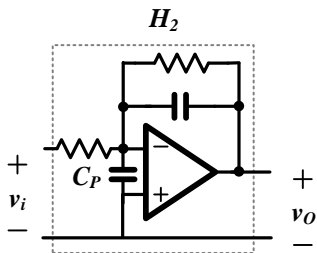- (d) Suppose the opamp has input capacitance as shown below. Compared to the transfer function in (b), What will happen to the magnitude of new H_2 as frequency is increased? [2pts]



$|H_2|$ (increases, **decreases**, stays the same) due to C_P . Confidence level ()