
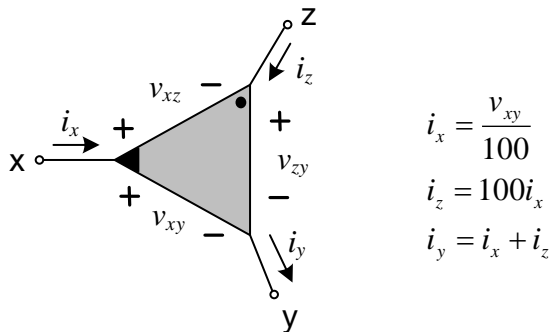


## Mid-Term Exam Solution

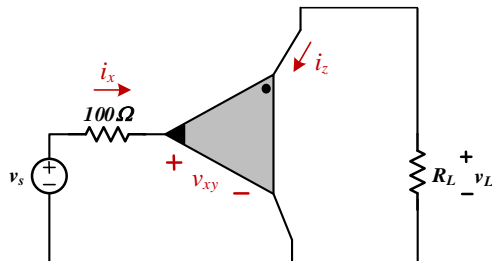1. **[Basic Circuit]** Consider the following 3-terminal device which has the following characteristics. [8pts]



- (a) Find  $v_L/v_s$  of the below circuit. [4pts]



(sol)

$$v_{xy} = v_s - 100 \cdot i_x = v_s - v_{xy} \rightarrow v_{xy} = \frac{v_s}{2}$$


$$i_z = 100 \cdot i_x = v_{xy} = \frac{v_s}{2}$$

$$v_L = (-i_z) \cdot R_L = \left(-\frac{v_s}{2}\right) \cdot R_L$$


$$\therefore \frac{v_L}{v_s} = -\frac{R_L}{2}$$

- (b) Draw an equivalent circuit model of the above device using one resistor and one dependent source. Specify the value of resistor and dependent source. [4pts]

(sol)

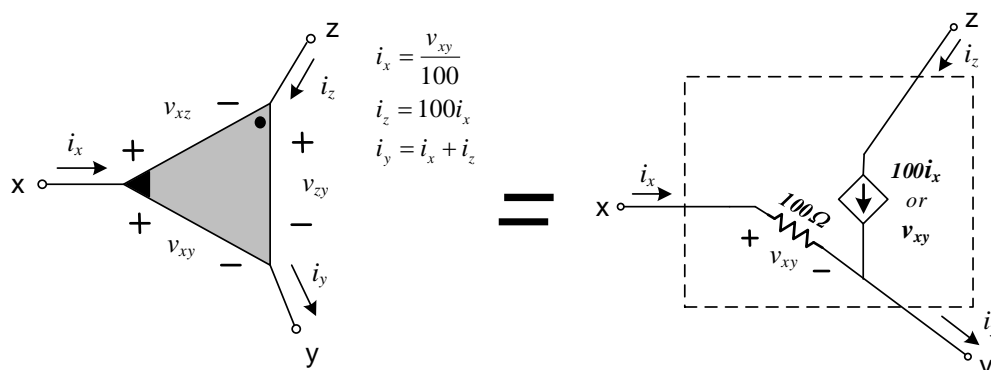

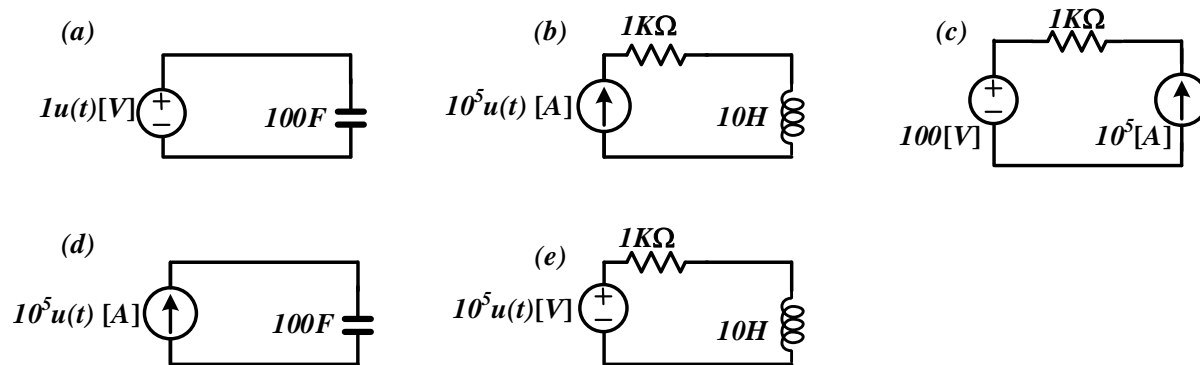2. Consider the circuits shown below. Which circuits are physically possible without damaging the wire? Assume that wire can handle current up to  $10^6\text{A}$ . [5pts]




ANS: C, D, E, \_\_\_\_\_, \_\_\_\_\_

A: Infinite current at  $t=0+$ ;

B: Infinite voltage at  $t=0+$ ;

3. Consider the circuit shown below. [12pts]

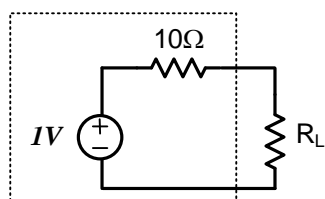- (a) Suppose the supply and the resistor in the dotted box represents a battery. What is the maximum power that can be drawn from this battery and what is the value of  $R_L$  for this condition? [2pts]



It is about the maximum power delivery question, not a maximum power efficiency.


Maximum power delivery:  $R_S=R_L \rightarrow R_L=10\Omega$ ,  $P_{\max\_drawn}=1/40\text{W}$

When the  $R_L$  is  $0\Omega$ , the power consumption of the battery is maximized. HOWEVER, the power is not to be DRAWN from the battery. The power is consumed by battery itself.

+ There are some vague terms, there can be a confusion.

If you see that the source is only a battery without  $R_S$  ( $10\Omega$ ), maximum power drawn happens at the  $R_L=0\Omega$ . So, we concede that the  $R_L=0\Omega$ , and it can be another correct answer. ( $R_L=0\Omega$ ,  $P_{\max}=1/10\text{W}$ )

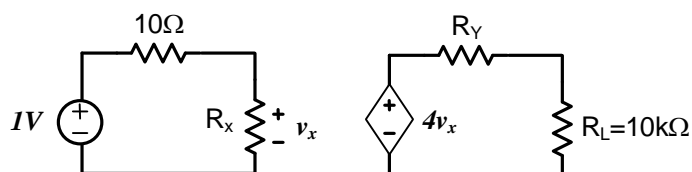- (b) Find values of  $R_X$  and  $R_Y$  between  $0.1\Omega \sim 1\text{M}\Omega$ , so that power is delivered to the load is maximum. [4pts]




For the maximum power delivery  $R_Y$  should be  $0.1\Omega$ .

To maximize dependent source at the second stage,  $v_x$  should be maximized.

Therefore, the first stage should have  $R_x$  as large as possible.  $R_x = 1\text{M}\Omega$ .

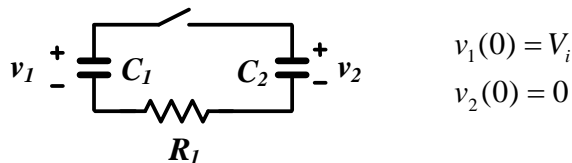For (c) and (d), consider the circuit shown below. The switch turns on at  $t=0$ . Assume that  $C_1$  and  $C_2$  have initial voltages of  $V_i$  and 0, respectively.



- (c) What should be the value of  $C_2$  and  $R_1$  such that maximum energy is delivered to  $C_2$  at steady-state? Express your answer using  $C_1$  and/or  $V_i$ . [3pts]

Initial charge:  $Q_{init} = V_i C_1$

Steady-stage charge = initial charge =  $Q_{init} = Q_{ss} = V_f (C_1 + C_2)$

Steady-stage Energy at  $C_2$  =  $E_{ss2} = \frac{1}{2} C_2 V_f^2 = \frac{1}{2} C_2 \cdot \left( \frac{C_1}{C_1 + C_2} V_i \right)^2$

$$\frac{dE_{ss2}}{dC_2} = \frac{C_1^2 V_i^2}{2} \cdot \frac{d}{dC_2} \frac{C_2}{(C_1 + C_2)^2} = \frac{C_1^2 V_i^2}{2} \cdot \frac{(C_1 + C_2)(C_1 + C_2 - 2C_1)}{(C_1 + C_2)^4}$$

$$\frac{dE_{ss2}}{dC_2} = 0 \quad \text{At } C_1 = C_2$$

Steady-stage energy will be maximized when the  $C_1$  is equal to  $C_2$ .

Energy delivery is independent to the  $R_1$ .

- (d) Suppose  $C_2 = 0.5C_1$  and the switch has a resistance of  $R_s$  when it is turned on. What is the energy lost through  $R_1$  and  $R_s$  as the circuit reaches steady-state? Express your answer using  $C_1$  and/or  $V_i$ . [3pts]


$$E_{init} = \frac{1}{2} C_1 V_i^2$$

$$E_{ss} = \frac{1}{2} (C_1 + C_2) V_f^2 = \frac{1.5}{2} C_1 V_f^2 = \frac{1.5}{2} C_1 \left( \frac{1}{1.5} V_i \right)^2 = \frac{1}{3} C_1 \cdot V_i^2$$

$$E_{lost} = E_{ss} - E_{init} = \frac{1}{6} C_1 \cdot V_i^2$$

It does not need to specify the lost energy at each resistor.

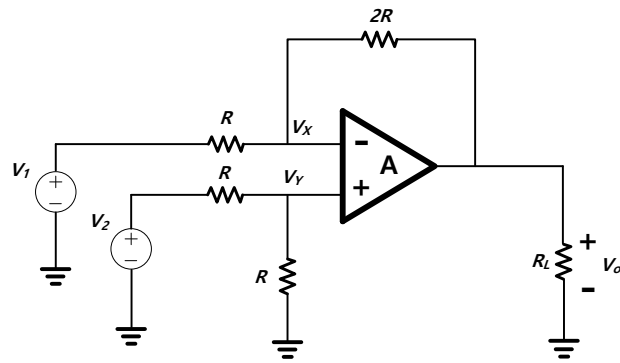For (a)~(c), consider the circuit shown below. [19pts]



- (a) Assume that the opamp is ideal. (i.e.  $A=\infty$ ). Express  $v_O$  in terms of  $v_1$  and  $v_2$ . [4pts]

sol)

$$V_o = -\frac{2R}{R}V_X + \left(1 + \frac{2R}{R}\right)(V_Y/2)$$

$$V_o = -2V_X + \frac{3}{2}V_Y$$

- (b) Suppose  $A < \infty$ . How does the gain  $|v_O/v_1|$  change compared to your answer in (a)? [2pts]

(i) Increases      (ii) Decreases      (iii) Stays the same


- (c) Suppose  $A < \infty$ . What is the relation between  $V_X$  and  $V_Y$ ? [2pts]

(i)  $V_X = V_Y$       (ii)  $V_X \neq V_Y$


- (d) Suppose  $A = \infty$  in the below circuit. How does the gain  $|v_O/v_X|$  change compared to your answer in (a) and what is the relation between  $V_X$  and  $V_Y$ ? [4pts]

- Gain  $|v_O/v_X|$ : (i) Increases      (ii) Decreases      (iii) Stays the same

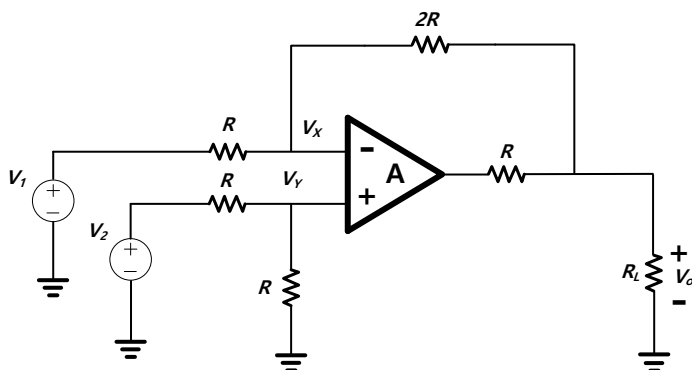- Relation between  $V_X$  and  $V_Y$ : (i)  $V_X = V_Y$       (ii)  $V_X \neq V_Y$



(e) Find the gain,  $|v_o/v_s|$  of the below circuit. [3pts]

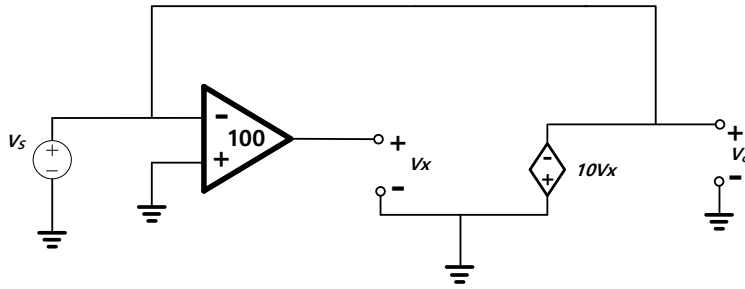

sol)

The problem has a contradiction.

(f) In this course, we learned a feedback circuit using an opamp that provides a voltage gain of 2. Why don't people just design an open-loop amplifier that has a gain of 2 without using feedback? Please fill in the below. [4pts]

In a feedback circuit, feedback factor( $\beta$ ) is \_\_\_\_\_ than 1 and thus, it can be made \_\_\_\_\_. The open-loop amplifier in the feedback circuit should have \_\_\_\_\_.

First blank: (i) smaller (ii) larger

Second blank: (i) very accurately (ii) with low power consumption (iii) with low-cost

Third blank: (i) large gain and high power consumption.


(ii) large gain and low power consumption.

(iii) small gain and low-power consumption


(iv) small and accurate gain

(v) large gain and can be inaccurate.

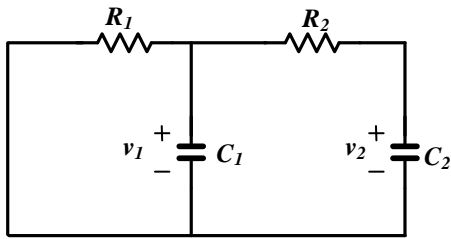4. Consider the circuit shown below [8pts]



- (a) Assume  $R_1=R_2=1\Omega$  and  $C_1=C_2=1F$ . Write down one differential equation for  $v_1$  that describes this circuit. (Do NOT include  $v_2$  in your equation.) [4pts]

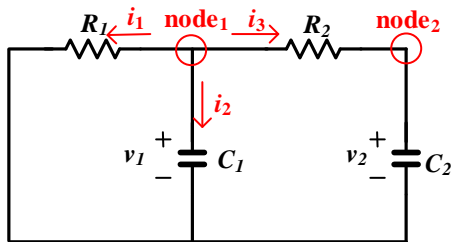

**Sol 1)**

[KCL 1]

$$i_1(t) + i_2(t) + i_3(t) = 0$$

$$(i_1(t) = v_1(t), i_2(t) = \dot{v}_1(t), \text{ and } i_3(t) = v_1(t) - v_2(t))$$

$$v_1(t) + \dot{v}_1(t) + v_1(t) - v_2(t) = 0$$

$$v_2(t) = 2v_1(t) + \dot{v}_1(t)$$

[KCL 2]

$$(v_2(t) - v_1(t)) + \dot{v}_2(t) = 0$$

$$(2v_1(t) + \dot{v}_1(t)) - v_1(t) + (2\dot{v}_1(t) + \ddot{v}_1(t)) = 0$$

$$\ddot{v}_1(t) + 3\dot{v}_1(t) + v_1(t) = 0$$

**Sol 2)**

[KCL]

$$i_1(t) + i_2(t) + i_3(t) = 0$$

$$(i_1(t) = v_1(t), i_2(t) = \dot{v}_1(t), \text{ and } i_3(t) = v_1(t) - v_2(t) = \dot{v}_2(t))$$

$$v_1(t) + \dot{v}_1(t) + \dot{v}_2(t) = 0 \quad \dots(1)$$

$$v_1(t) + \dot{v}_1(t) + v_1(t) - v_2(t) = 0 \quad \dots(2)$$


By taking derivative to the equation (2),

$$2\dot{v}_1(t) + \ddot{v}_1(t) - \dot{v}_2(t) = 0 \quad \dots(2')$$


By adding (1) and (2'),

$$\ddot{v}_1(t) + 3\dot{v}_1(t) + v_1(t) = 0$$

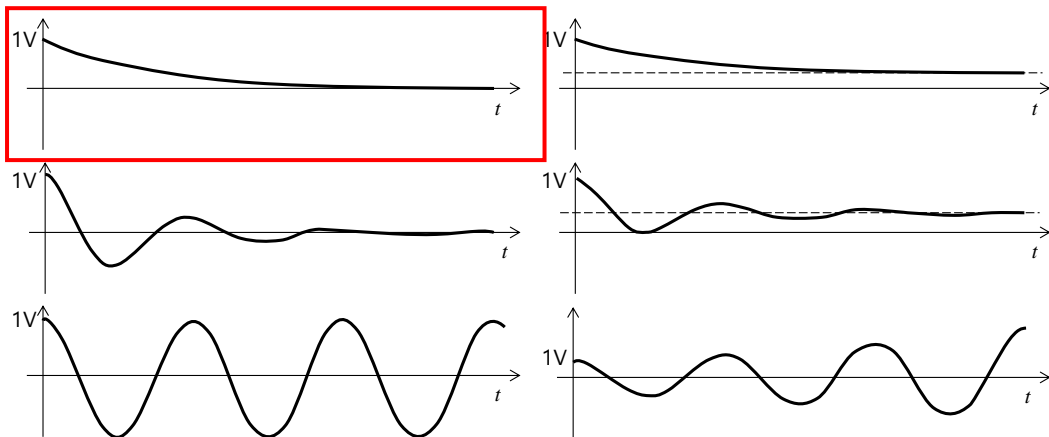
(b) Suppose there is initial voltage of 1V on  $C_1$  and 0V on  $C_2$ . Which of the below can be a solution to this circuit?[2pts]



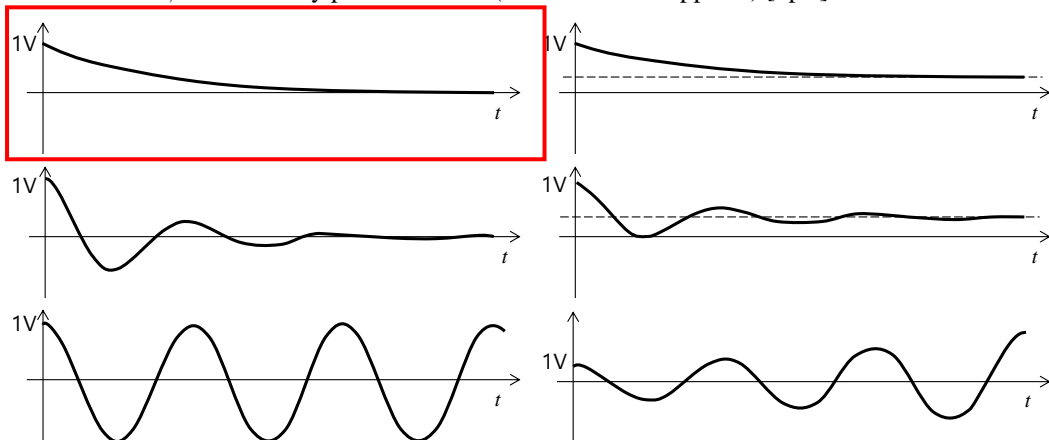(c) Suppose there is initial voltage of 1V on  $C_1$  and 0V on  $C_2$ . Which of the below can be a solution to this circuit if  $R_1$ ,  $R_2$  and  $C_1, C_2$  can be any positive value. (Choose all that applies.) [2pts]



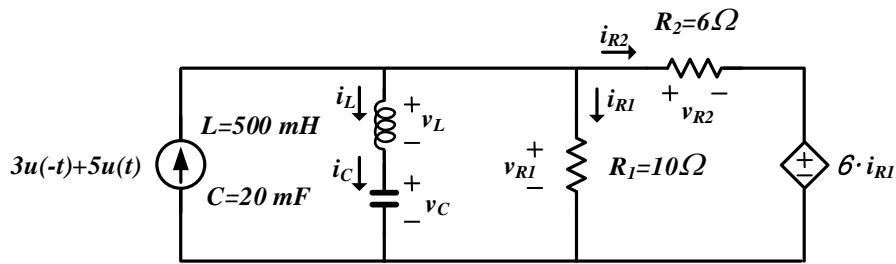5. Consider the circuit shown below. [16pts]



(a) Fill in the table below. [8pts]

$v_L(0^-)$	$i_L(0^-)$	$v_{R1}(0^-)$	$v_C(0^-)$
<b>0</b>	<b>0</b>	<b>18</b>	<b>18</b>
$i_{R1}(0^-)$	$i_C(0^+)$	$i_{R1}(0^+)$	$i_{R2}(0^+)$
<b>1.8</b>	<b>0</b>	<b>3</b>	<b>2</b>
$v_C(0^+)$	$v_{R1}(0^+)$	$v_{R2}(0^+)$	$v_L(0^+)$
<b>18</b>	<b>30</b>	<b>12</b>	<b>12</b>
$\frac{dv_C}{dt}(0^+)$	$\frac{di_L}{dt}(0^+)$	$\frac{di_{R1}}{dt}(0^+)$	$\frac{di_{R2}}{dt}(0^+)$
<b>0</b>	<b>24</b>	<b>-14.4</b>	<b>-9.6</b>

(b) Find  $i_L(t)$  for  $t > 0$ . [6pts]

$$R_{th} = 6$$

$$\alpha = \frac{R_{th}}{2L} = 6, \omega_0 = \frac{1}{\sqrt{LC}} = 10$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 8$$

$$i_L(t) = e^{-\alpha t}(B_1 \cos \omega_d t + B_2 \sin \omega_d t) + I_F$$

$$i_L(\infty) = 0 = I_F$$

$$i_L(0^+) = e^{-\alpha \cdot 0}(B_1 \cos \omega_d \cdot 0 + B_2 \sin \omega_d \cdot 0) + I = 0 = B_1$$

$$B_1 = 0$$

$$v_L(0^+) = R_{th} \times (5 - 3) = L \left. \frac{di_L}{dt} \right|_{t=0^+} = L \omega_d B_2 \cos \omega_d t \big|_{t=0^+} = L \omega_d B_2$$

$$B_2 = \frac{R_{th} \times (5 - 3)}{L \omega_d} = 3$$

$$i_L(t) = e^{-6t}(3 \sin 8t)$$


(c) What kind of response does this circuit have? [2pts]

(i) Overdamped (ii) **Underdamped** (iii) Critically-damped




7. Assume that the opamp is ideal and initial charge of the capacitor is 0. [15pts]

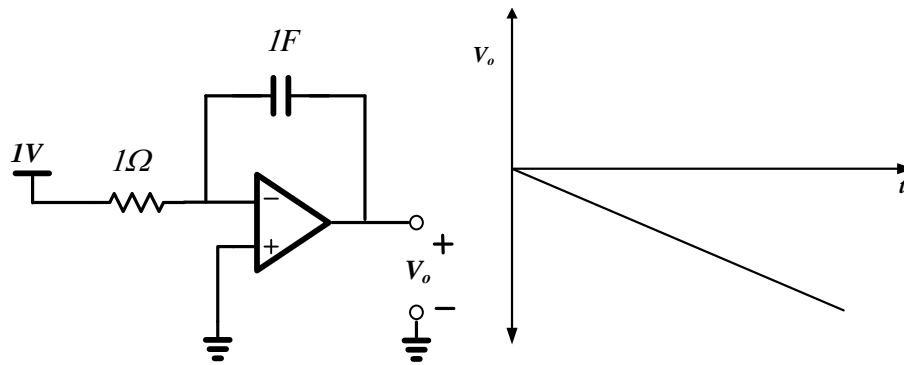(a) Sketch  $V_o(t)$  for  $t > 0$ . [4pts]



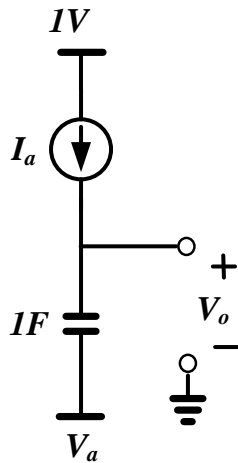
(b) Find the values of  $V_a$  and  $I_a$  such that the above two circuits are identical. [4pts]



Sol)  $V_a = 0V$ ,  $I = -1 A$

(c) Suppose that the opamp has finite gain of  $G$ . Derive an expression of  $V_o(t)$  as a function of  $G$ . [7pts]

Sol)

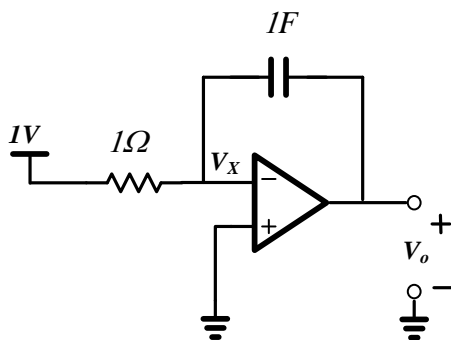

$$G(0 - V_X) = V_o \quad \dots \textcircled{1}$$

$$\frac{1 - V_X}{1} = C \cdot \frac{d(V_X - V_o)}{dt} \quad \dots \textcircled{2}$$

$$1 + \frac{1}{G}V_o = -\left(\frac{1}{G} + 1\right) \frac{dV_o}{dt}$$

$$\left(\frac{1}{G} + 1\right) \frac{dV_o}{dt} + \frac{1}{G}V_o + 1 = 0$$


$$\therefore V_o = G(e^{-\frac{t}{(G+1)}} - 1)$$

8. Assume that the opamp is ideal and initial charge of the capacitor is 0 [10pts] (Hint: Use 7(b))

A. What is the time-constant of the below circuit? [2pts]


B. Find the values of  $v_o(0)$  and  $v_o(\infty)$  [4pts]

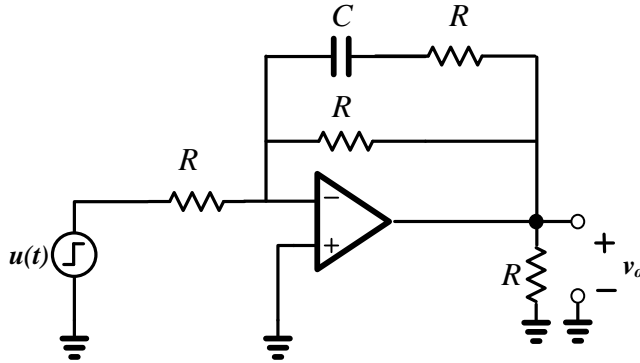C. Find an expression for  $v_o(t)$ . Assume that initial charge on the capacitor is 0. [4pts]



Sol)

(a)

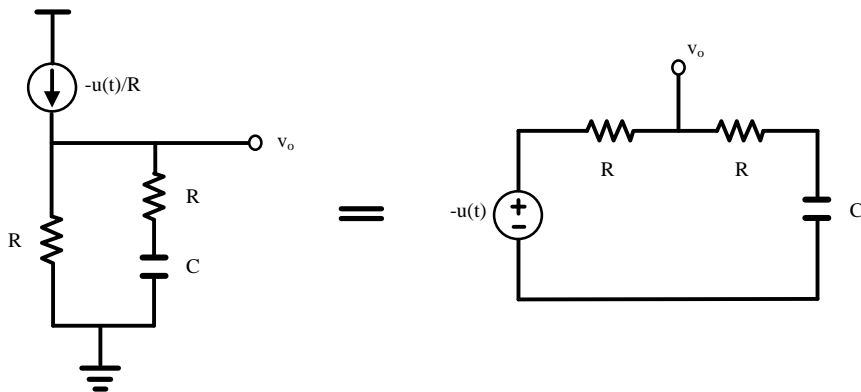

Time constant =  $C \times (R+R) = 2RC$

(b)

$$v_o(0^-) = 0V, v_o(0^+) = -1/2V$$

$$v_o(\infty) = -1V$$

(c)

Let's denote the voltage of node between C capacitor and R resistor as  $v_x$ .

KCL:

$$-\frac{u(t)}{R} + C \frac{d}{dt}(-v_x) + \frac{-v_o}{R} = 0 \quad - \textcircled{1}$$

$$C \frac{dv_x}{dt} + \frac{v_x - v_o}{R} = 0 \quad - \textcircled{2}$$

Substitute ② into ① then you get the following eq.

$$-\frac{u(t)}{R} + \frac{v_x - v_o}{R} + \frac{-v_o}{R} = 0$$

$$\Rightarrow v_x = 2v_o + u(t)$$

Substitute this eq. into ②

$$C \frac{d}{dt} (2v_o + v_{in}) + \frac{v_o + v_{in}}{R} = 0$$

$$\Rightarrow \frac{d}{dt} v_o + \frac{v_o}{2RC} = -\frac{v_{in}}{2RC}$$


The general eq. for output voltage is

$$v_o = A e^{-\frac{t}{2RC}} + B$$


From the answers to (b), we can decide the values of A and B.

$$v_o = \left( \frac{1}{2} e^{-\frac{t}{2RC}} - 1 \right) u(t)$$

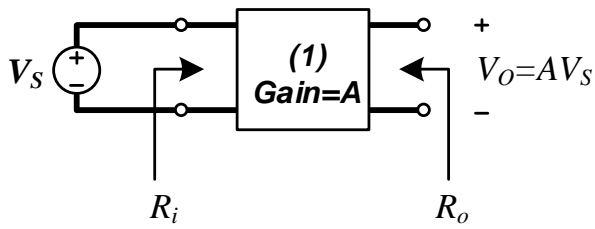
9. Consider the below system which has a voltage gain of A and some input and output resistances. [7pts]



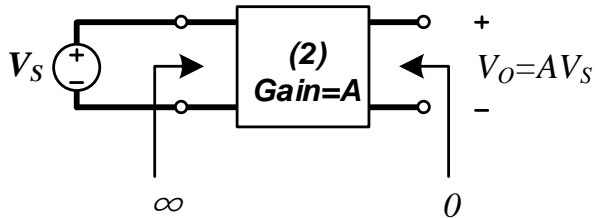
$$\text{Cascaded Gain} = A \cdot \left( \frac{R_i}{R_i + R_o} \right) \cdot A$$



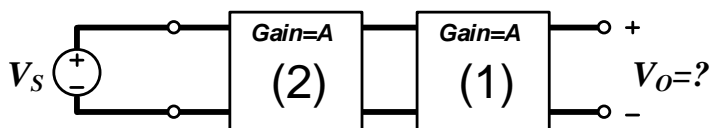
Find the gain of the below cascaded networks. Express your answer using A,  $R_i$  and  $R_o$ .


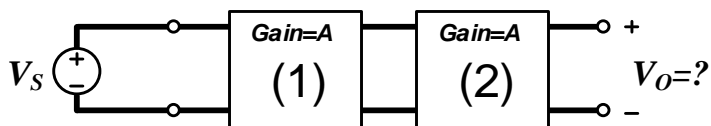
$$V_o = A^2 \left( \frac{R_i}{R_i + 0} \right) V_i = A^2 V_i$$


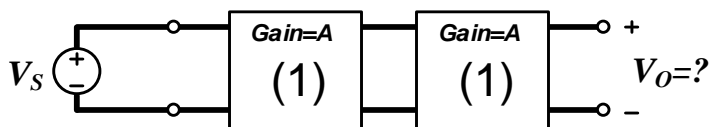
$$V_o = A^2 \left( \frac{\infty}{\infty + R_o} \right) V_i = A^2 V_i$$



$$V_o = A^2 \left( \frac{R_i}{R_i + R_o} \right) V_i$$

학번(ID): \_\_\_\_\_ 이름(Name): \_\_\_\_\_

#1	#2	#3	#4	#5	#6	#7	#8	#8	Total
/8	/5	/12	/19	/8	/16	/15	/10	/7	/100