

## Quiz #2 [Solution]

### 1. Phasor and Complex numbers [6pts]

- (a) Suppose  $v_1(t) = \cos(10^3t + 60^\circ)$ . Let's represent this signal as  $\mathbf{V}_1 = 1 \angle 0^\circ$ . If  $\mathbf{V}_2 = 0.5 \angle 10^\circ$ , then what is  $v_2(t)$ ?



Sol)  $v_1(t) = 0.5\cos(10^3t + 70^\circ)$

- (b) Suppose  $v_1(t) = \cos(10^3t + 60^\circ)$ . Let's represent this signal as  $\mathbf{V}_1 = 1 + j$ . If  $v_2(t) = \cos(10^3t + 105^\circ)$ , then what is  $\mathbf{V}_2$ ?


Sol)  $v_1(t) = \cos(10^3t + 60^\circ) \rightarrow \mathbf{V}_1 = 1 + j = \sqrt{2} \angle 45^\circ$

$\therefore v_2(t) = \cos(10^3t + 105^\circ) \rightarrow \mathbf{V}_2 = \sqrt{2} \angle 90^\circ = \sqrt{2} j$
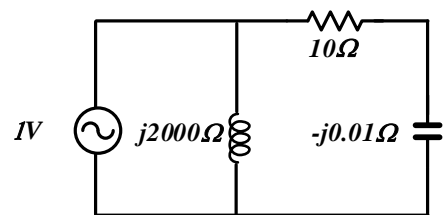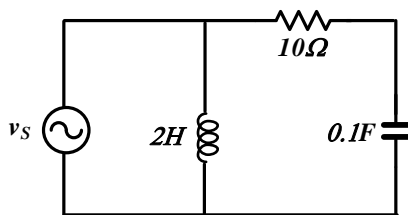
### 2. Represent the impedance of each circuit component in complex numbers when $v_s = \cos(10^3t)$ . [10pts]


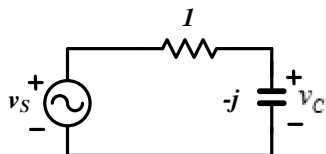
### 3. Find the sinusoidal steady-state voltage, $v_C(t)$ , of the below circuit, when $v_s = \cos(10^3t)$ . Express your answer in time-domain. [10pts]



Sol)

$$\mathbf{V}_C = \mathbf{V}_s * (-j)/(1-j)$$

$$= 1 \angle 0^\circ * 1/\sqrt{2} \angle -45^\circ$$

$$v_C = (1/\sqrt{2}) * \cos(10^3t - 45^\circ)$$

4. Suppose the sinusoid voltage and current of a load is represented using the below vectors. Note that the magnitude of the vectors represents the **rms** values. [16pts]

- (a) What are the apparent power, average power and power factor? [9pts]

Complex power:  $\mathbf{S} = \mathbf{V}_{rms} \mathbf{I}_{rms}^*$

Apparent power:  $|\mathbf{S}| = V_{rms} I_{rms}$

$$\mathbf{V}_{rms} = 2 + 2j, \rightarrow V_{rms} = \sqrt{4+4} = \sqrt{8}$$

$$\mathbf{I}_{rms} = 2 + j, \rightarrow I_{rms} = \sqrt{4+1} = \sqrt{5}$$

$$\text{Apparent power} = |\mathbf{S}| = |\mathbf{V}_{rms}| \cdot |\mathbf{I}_{rms}| = 2\sqrt{2} \cdot \sqrt{5} = 2\sqrt{10}$$

$$\text{Average power} = P = \overrightarrow{V_{rms}} \cdot \overrightarrow{I_{rms}} = (2, 2) \cdot (2, 1) = 6$$

$$\text{Power factor} = PF = \frac{P}{|\mathbf{S}|} = \frac{6}{2\sqrt{10}} = \frac{3}{\sqrt{10}} = 0.3\sqrt{10}$$

- (b) How will the above answer change if the vector represents the amplitude and not the rms value? [3pts]


$$\frac{V_m}{\sqrt{2}} = V_{rms}, \quad \frac{I_m}{\sqrt{2}} = I_{rms}$$

$$\text{Apparent power} = |\mathbf{S}| = |\mathbf{V}_{rms}| \cdot |\mathbf{I}_{rms}| = \sqrt{10}$$

$$\text{Average power} = P = 2 + 1 = 3$$

$$\text{Power factor} = PF = \frac{P}{|\mathbf{S}|} = \frac{3}{\sqrt{10}} = 0.3\sqrt{10}$$

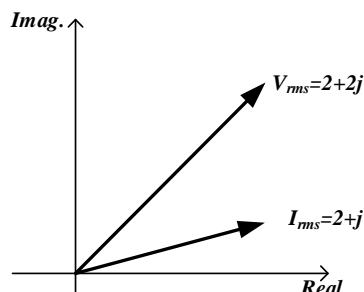- (c) What is the voltage vector that is needed to achieve a power factor of 1? [4pts]



**Sol 1>**  $V_{rms} = k(2 + j)$  , k can be any number.

In the case with the same apparent power:

$$\sqrt{5k^2} = \sqrt{8} \rightarrow k = \sqrt{\frac{8}{5}}$$


$$\text{So } V_{rms} = \sqrt{\frac{8}{5}}(2 + j) = \frac{4\sqrt{10}}{5} + \frac{2\sqrt{10}}{5}j$$

<Sol 2>

Insert power factor correction vector

$\therefore V_{corr} = -j$

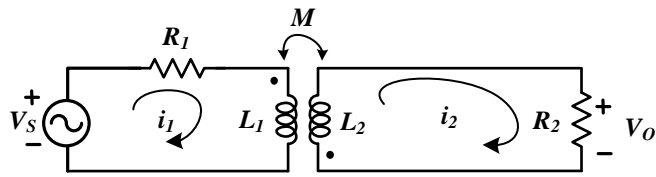5. Consider the circuit shown below. [8pts]



- (a) Suppose  $v_s(t) = \cos(10^3 t)$ . Write down two equations that can be used to analyze the above circuit. You may write the equations in differential form.

Sol)

$$v_s = i_1 \cdot R_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$i_2 \cdot R_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} = 0$$

- (b) Suppose  $V_s = 1 \text{ V}$ . Express the steady-state voltage  $V_o$  in terms of  $R_1$ ,  $R_2$ ,  $L_1$ ,  $L_2$  and  $M$ .

Sol)

$$\text{DC input} = \frac{di_1}{dt} = 0$$

$$V_o = 0 \text{ V}$$