


Quiz #1 [50pts] **Solution**

1. Which of the below system(s) is(are) linear? [5pts] **ANS: (a , b , c)**



(a) $i(t) = \frac{d^3 v(t)}{dt^3}$: input = $v(t)$, output = $i(t)$ **:Linear**

(b) $v(t) = 4i(t) + 3$: input = $i(t)$, output = $v(t) - v(0)$ **:Linear**

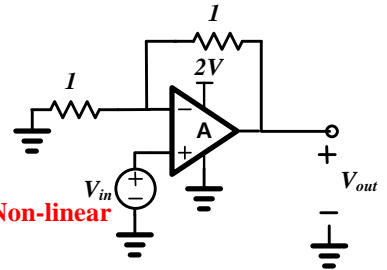
(c) Circuit shown in right with a practical opamp where input: $V_{in}(t)$, output: $V_{out}(t)$ **:Non-linear**



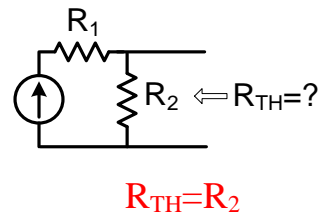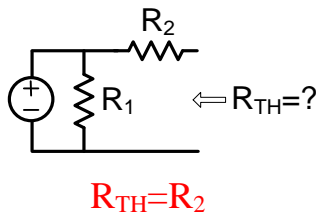
2. What is the resistance (R_{TH}) seen in the below circuits? (i.e. find the Thevinin resistance) [8pts]



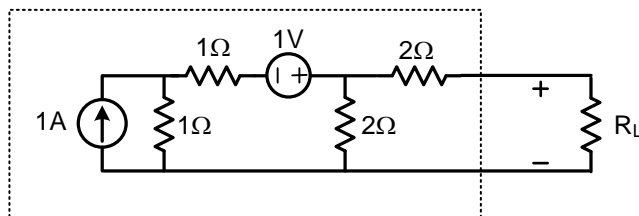
3. Consider the circuit shown below. [10pts]



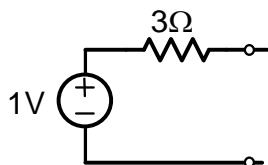(a) Draw the Thevenin equivalent of the circuit in the dotted box. [4pts]



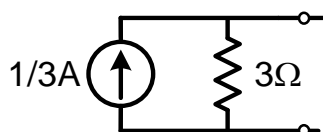
(b) Draw the Norton equivalent of the circuit in the dotted box. [2pts]



(c) What value of load resistance would result in the maximum power delivered to the load? [4pts]

$R_L = 3\Omega$

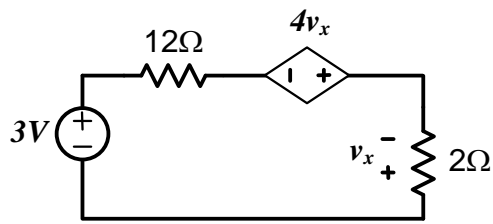4. What is the power absorbed by the $2\ \Omega$ resistor in the circuit shown below? [8pts]




$$\text{Eq1. } 3 - 12i + 4v_x - 3i = 0$$

$$\text{Eq2. } v_x = -2i$$

$$\therefore i = 3/22\text{ A,}$$

$$\text{Power} = I^2 R = 9/242 \approx 0.0372\text{ W}$$

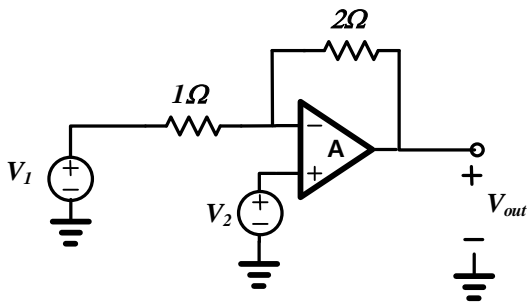5. Express V_{out} as a function of V_1 and V_2 . Assume that the opamp is ideal. [8pts]



$$\frac{(V_1 - V_2)}{1} = \frac{(V_2 - V_{out})}{2}$$

$$V_{out} = -2V_1 + 3V_2$$

6. In order for KCL to hold, length of wire must be sufficiently (**short**, long). Moreover, the speed of electrons must be (equal to speed of light, close to speed of light, slower than speed of light, **depends on the condition**).

[5pts]

7. How would you compare the magnitude of A and β to 1 in a feedback system? [6pts] (e.g. $100 \gg 1$, $\beta > 1$)

$$A \quad (>>) \quad > \quad \cong \quad < \quad (<<) \quad 1$$

$$\beta \quad (>>) \quad > \quad \cong \quad < \quad (<<) \quad 1$$