
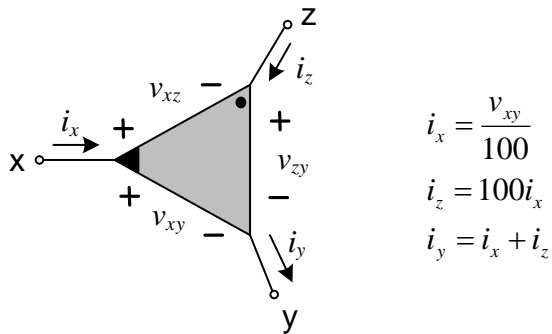


Mid-Term Exam (3 hours)

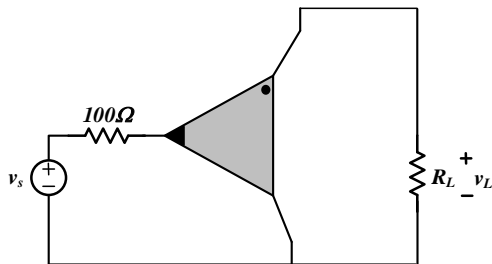1. **[Basic Circuit]** Consider the following 3-terminal device which has the following characteristics. [8pts]








- (a) Find v_L/v_s of the below circuit. [4pts]



- (b) Draw an equivalent circuit model of the above device using one resistor and one dependent source. Specify the value of resistor and dependent source. [4pts]

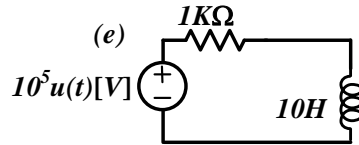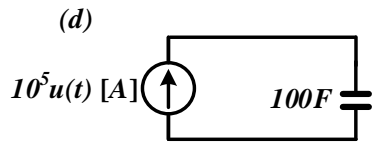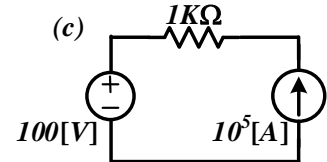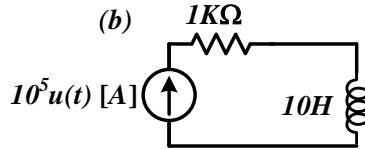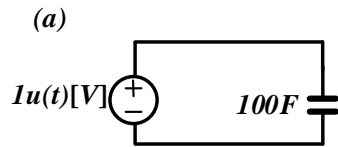
2. Consider the circuits shown below. Which circuits are physically possible without damaging the wire? Assume that wire can handle current up to 10^6A . [5pts]




ANS: _____, _____, _____, _____, _____

3. Consider the circuit shown below. [12pts]

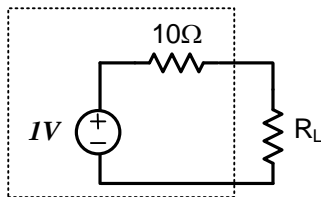
- (a) Suppose the supply and the resistor in the dotted box represents a battery. What is the maximum power that can be drawn from this battery and what is the value of R_L for this condition? [2pts]



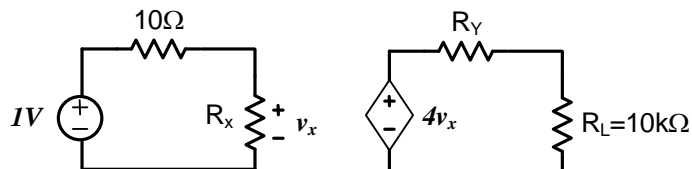- (b) Find values of R_X and R_Y between $0.1\Omega \sim 1\text{M}\Omega$, so that power is delivered to the load is maximum. [4pts]



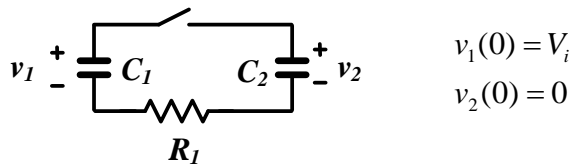
For (c) and (d), consider the circuit shown below. The switch turns on at $t=0$. Assume that C_1 and C_2 have initial voltages of V_i and 0, respectively.



- (c) What should be the value of C_2 and R_1 such that maximum energy is delivered to C_2 at steady-state? Express your answer using C_1 and/or V_i . [3pts]

- (d) Suppose $C_2 = 0.5C_1$ and the switch has a resistance of R_s when it is turned on. What is the energy lost through R_1 and R_s as the circuit reaches steady-state? Express your answer using C_1 and/or V_i . [3pts]

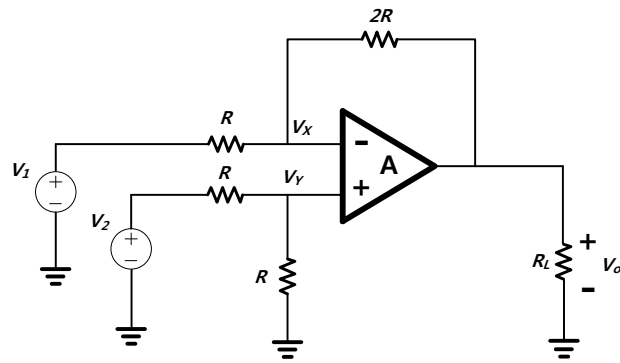4. For (a)~(c), consider the circuit shown below. [19pts]



(a) Assume that the opamp is ideal. (i.e. $A=\infty$). Express v_o in terms of v_1 and v_2 . [4pts]

(b) Suppose $A < \infty$. How does the gain $|v_o/v_1|$ change compared to your answer in (a)? [2pts]

- (i) Increases (ii) Decreases (iii) Stays the same


(c) Suppose $A < \infty$. What is the relation between V_x and V_y ? [2pts]

- (i) $V_x = V_y$ (ii) $V_x \neq V_y$


(d) Suppose $A = \infty$ in the below circuit. How does the gain $|v_o/v_x|$ change compared to your answer in (a) and what is the relation between V_x and V_y ? [4pts]

- Gain $|v_o/v_x|$: (i) Increases (ii) Decreases (iii) Stays the same

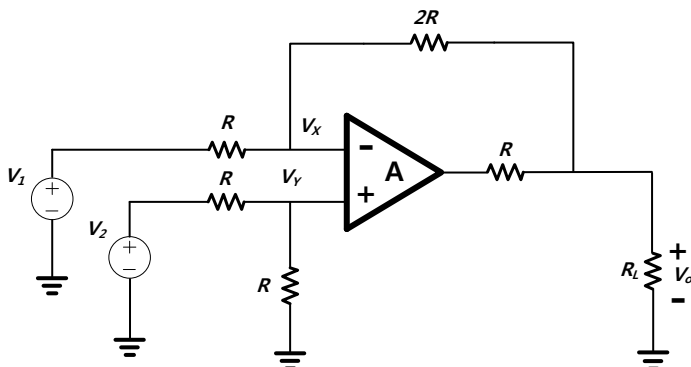- Relation between V_x and V_y : (i) $V_x = V_y$ (ii) $V_x \neq V_y$



(e) Find the gain, $|v_o/v_s|$ of the below circuit. [3pts]

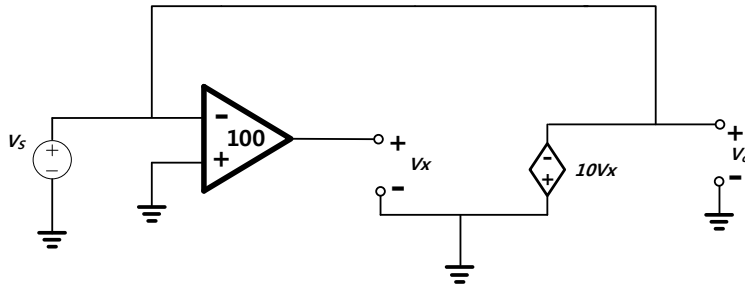

(f) In this course, we learned a feedback circuit using an opamp that provides a voltage gain of 2. Why don't people just design an open-loop amplifier that has a gain of 2 without using feedback? Please fill in the below. [4pts]

In a feedback circuit, feedback factor(β) is _____ than 1 and thus, it can be made _____. The open-loop amplifier in the feedback circuit should have _____.

First blank: (i) smaller (ii) larger

Second blank: (i) very accurately (ii) with low power consumption (iii) with low-cost

Third blank: (i) large gain and high power consumption.


(ii) large gain and low power consumption.

(iii) small gain and low-power consumption

(iv) small and accurate gain


(v) large gain and can be inaccurate.

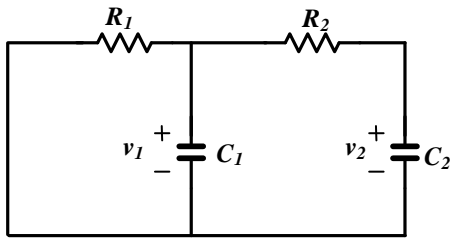5. Consider the circuit shown below [8pts]




- (a) Assume $R_1=R_2=1\Omega$ and $C_1=C_2=1F$. Write down one differential equation for v_1 that describes this circuit. (Do NOT include v_2 in your equation.) [4pts]

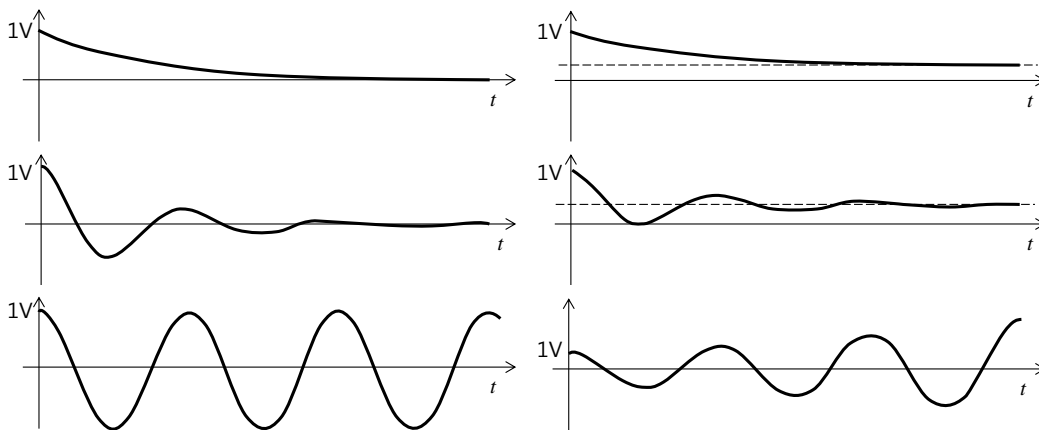
- (b) Suppose there is initial voltage of 1V on C_1 and 0V on C_2 . Which of the below can be a solution to this circuit?[2pts]



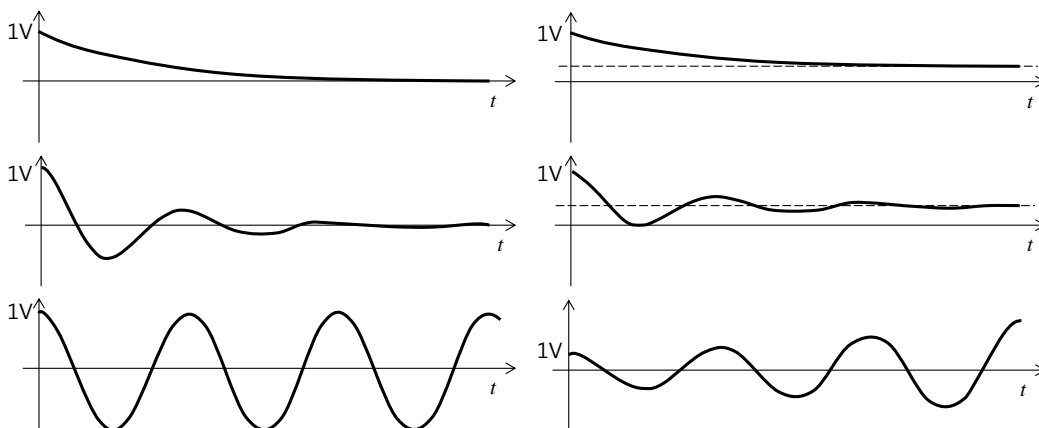- (c) Suppose there is initial voltage of 1V on C_1 and 0V on C_2 . Which of the below can be a solution to this circuit if R_1 , R_2 and C_1 , C_2 can be any positive value. (Choose all that applies.) [2pts]



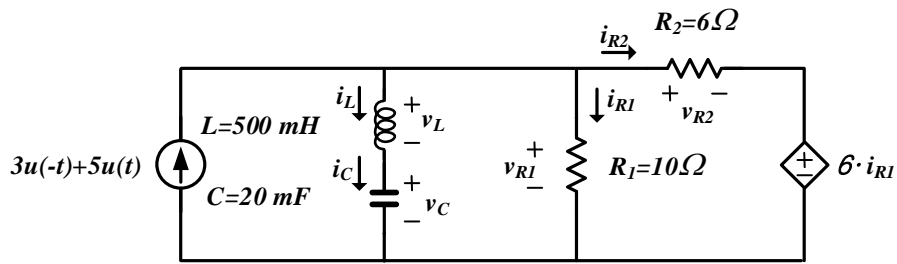6. Consider the circuit shown below. [16pts]



(a) Fill in the table below. [8pts]

$v_L(0^-)$	$i_L(0^-)$	$v_{R1}(0^-)$	$v_C(0^-)$
$i_{R1}(0^-)$	$i_C(0^+)$	$i_{R1}(0^+)$	$i_{R2}(0^+)$
$v_C(0^+)$	$v_{R1}(0^+)$	$v_{R2}(0^+)$	$v_L(0^+)$
$\frac{dv_C}{dt}(0^+)$	$\frac{di_L}{dt}(0^+)$	$\frac{di_{R1}}{dt}(0^+)$	$\frac{di_{R2}}{dt}(0^+)$


(b) Find $i_L(t)$ for $t > 0$. [6pts]

(c) What kind of response does this circuit have? [2pts]


(i) Overdamped (ii) Underdamped (iii) Critically-damped

7. Assume that the opamp is ideal and initial charge of the capacitor is 0. [15pts]

(a) Sketch $V_o(t)$ for $t > 0$. [4pts]

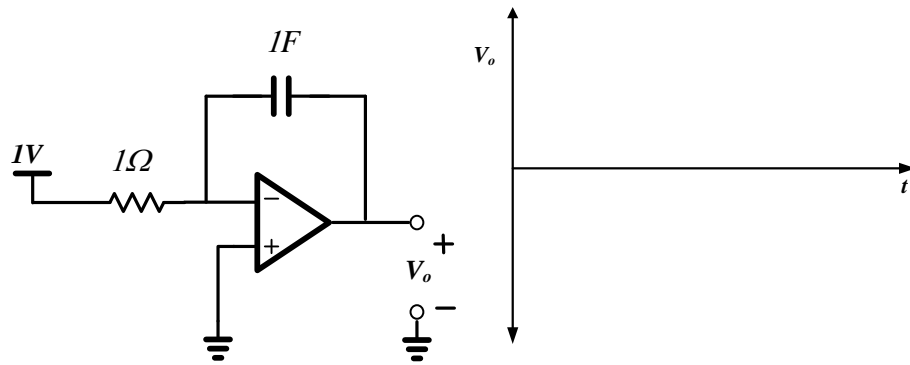

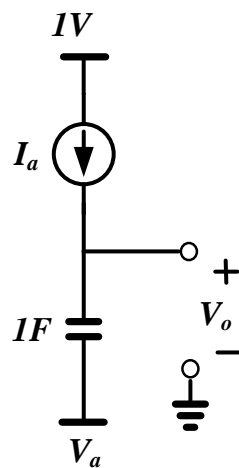(b) Find the values of V_a and I_a such that the above two circuits are identical. [4pts]




(c) Suppose that the opamp has finite gain of G . Derive an expression of $V_o(t)$ as a function of G . [7pts]

8. Assume that the opamp is ideal and initial charge of the capacitor is 0 [10pts] (Hint: Use 7(b))



(a) What is the time-constant of the below circuit? [2pts]

(b) Find the values of $v_o(0)$ and $v_o(\infty)$ [4pts]



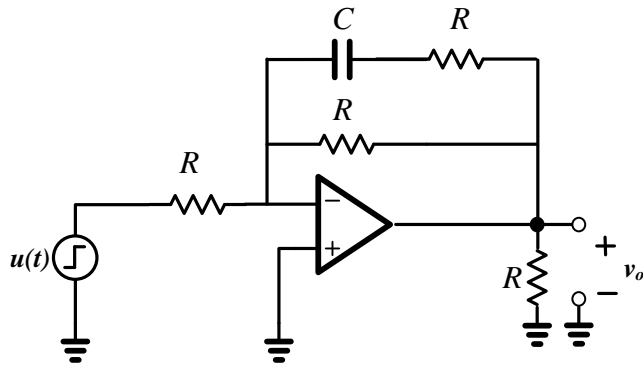
(c) Find an expression for $v_o(t)$. Assume that initial charge on the capacitor is 0. [4pts]



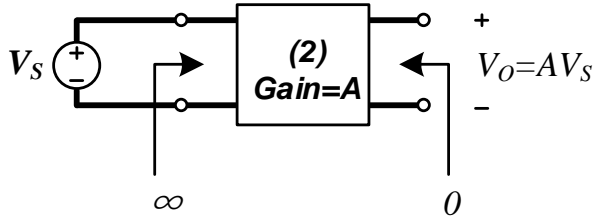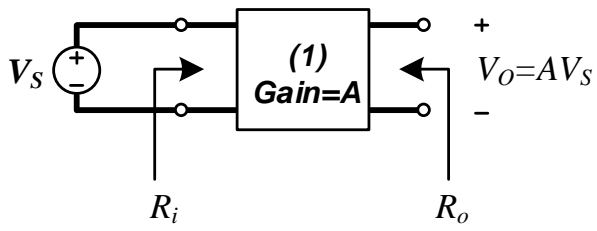9. Consider the below system which has a voltage gain of A and some input and output resistances. [7pts]



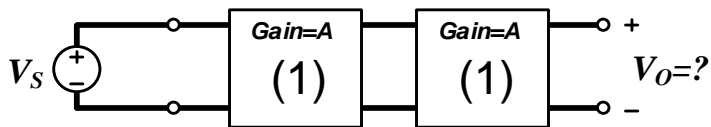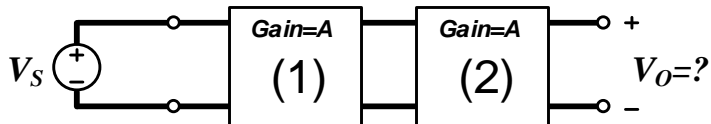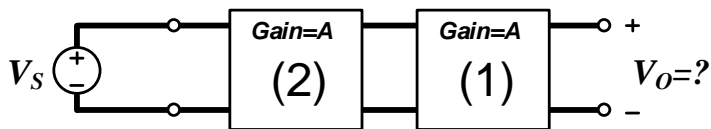Find the gain of the below cascaded networks. Express your answer using A, R_i and R_o .



학번(ID): _____ 이름(Name): _____

#1	#2	#3	#4	#5	#6	#7	#8	#8	Total
/8	/5	/12	/19	/8	/16	/15	/10	/7	/100