


IMPORTANT: Assume all circuit elements are ideal. Unless otherwise specified, all answers must be correct to four decimal places. All answers must be with proper units.

Question 1. (10 points) Evaluate the expressions below. (2 points each). You must answer with the simplest and most proper unit for each expression.


- a) $(5 \text{ mA}) / (4 \text{ V})$
- b) $\text{Im}[(4\angle 30^\circ \text{ V}_{\text{rms}})^2 / (3\angle 120^\circ \Omega)]$
- c) $[(50 \mu\text{H}) \times (20 \text{ nF})]^{1/2}$
- d) $(3 \text{ mV})^2 \times (5 \text{ mF})$
- e) $(10 \text{ k}\Omega) / (5 \mu\text{H})$

Question 2. (10 points) Find the equivalent resistance of each circuit. Every resistor in the circuits has a resistance of $1 \text{ k}\Omega$.


- a) (2 points)

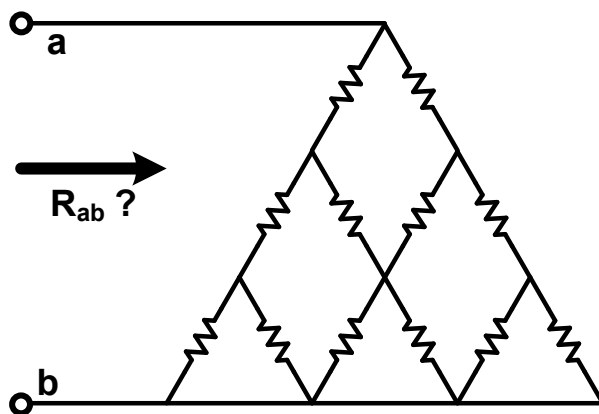

- b) (3 points)

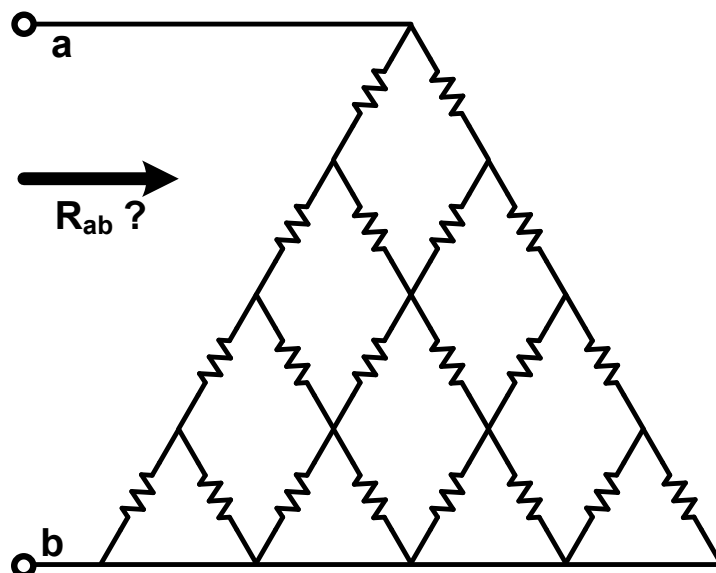


c) (5 points)

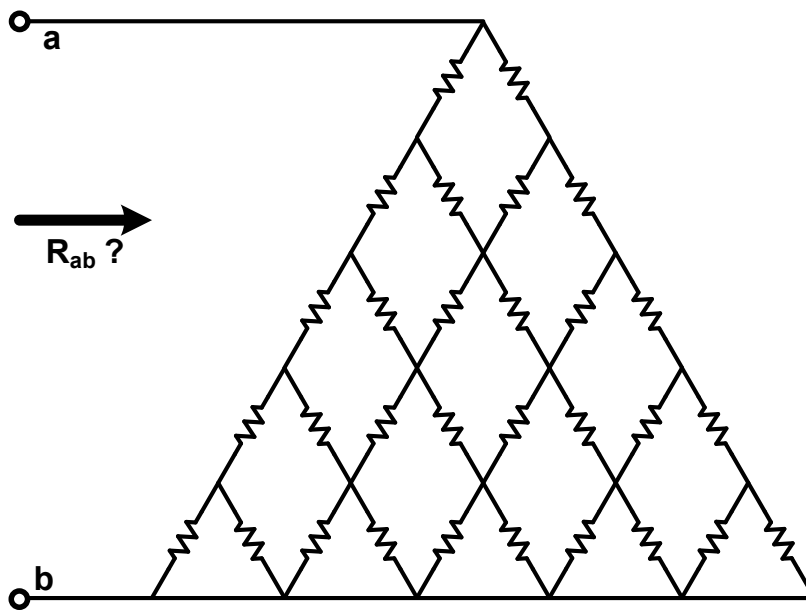


Question 3. (10 points) Analyze the circuits below and answer the questions.

a) Find V_o in the circuit below.

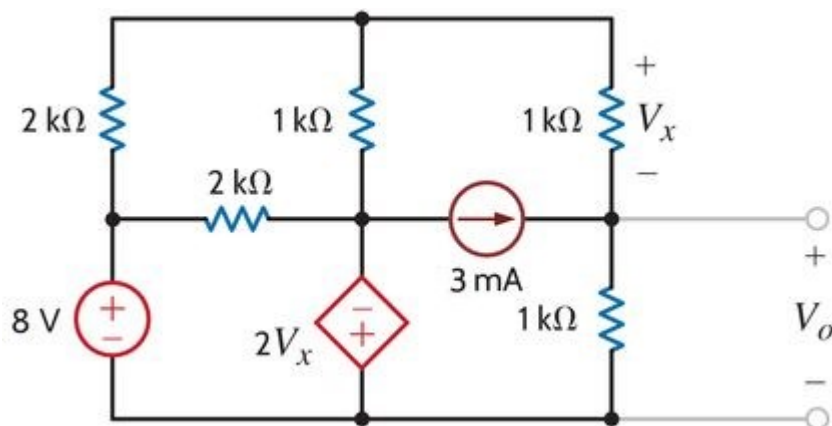


b) Find R_L for maximum power transfer and the maximum power dissipated in R_L .

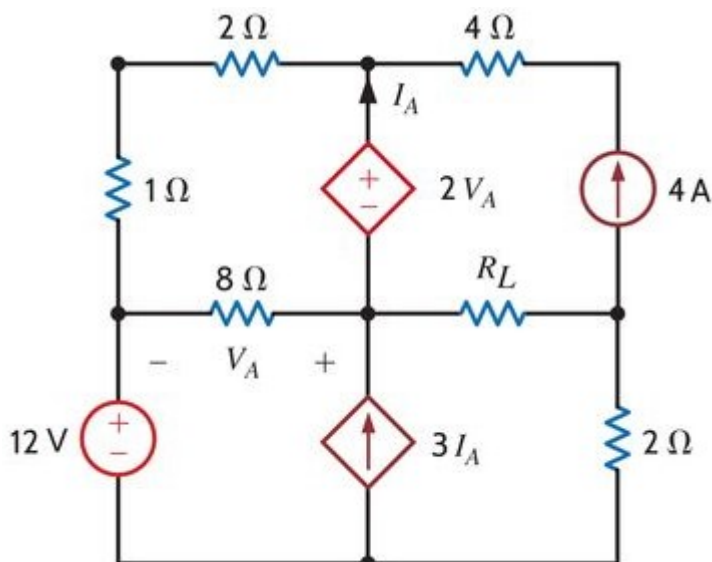


Question 4. (10 points)

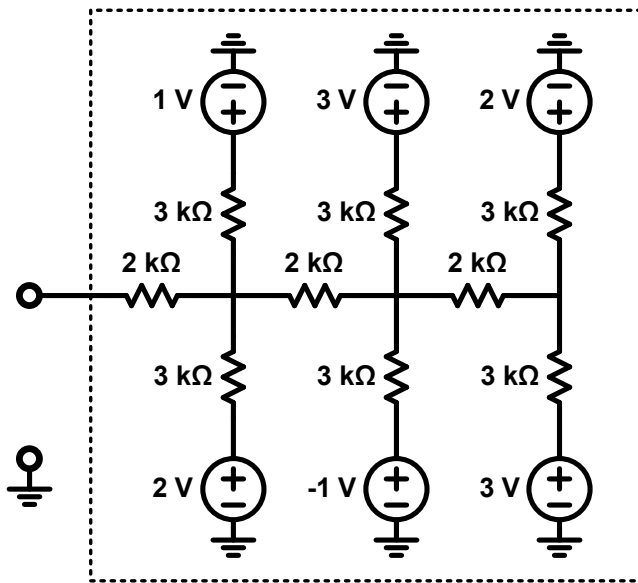
- a) (4 points) Find the Thevenin equivalent circuit of the circuit below (answer must include open circuit voltage and Thevenin equivalent resistance).



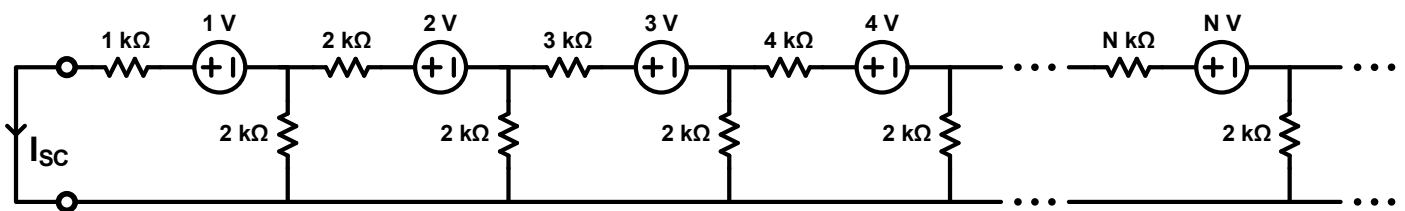
- b) (6 points) Find the short circuit current (I_{sc}) of the circuit below.




Question 5. (10 points) Design an op-amp circuit such that $V_o = V_1 + 2V_2 + 3V_3 - 4\frac{d}{dt}V_1$. Use op-amps, resistors, capacitors, and inductors only. **Do not** use more than 2 op-amps, and only designs with one op-amp can get full points. (You can get max. 5 points with a design with 2 op-amps)

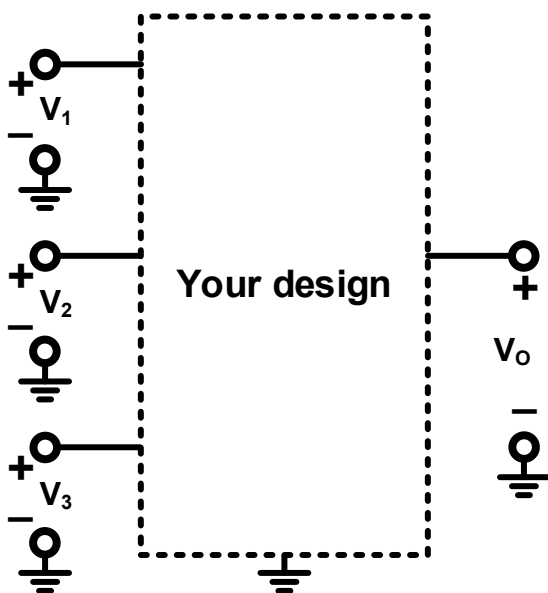

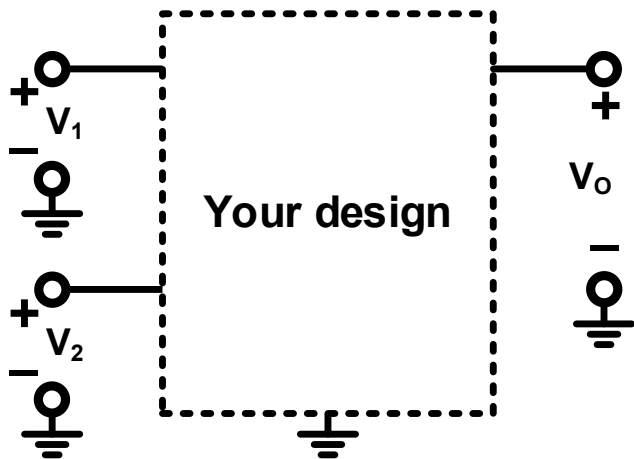
Question 6. (7 points) Prove or disprove: Can we design an op-amp circuit such that $V_o = V_1 \times V_2$, using op-amps, resistors, capacitors, and inductors only? Assume all elements are ideal.



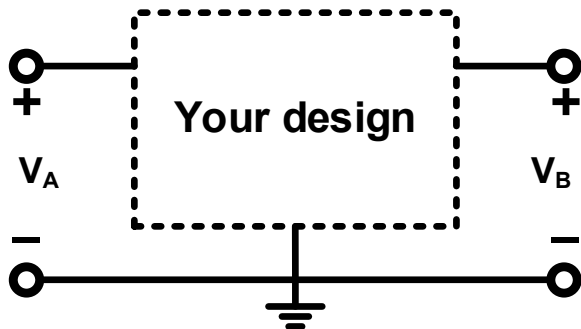Question 7. (5 points) By using resistors, capacitors, and inductors only, design a circuit that acts as a low-pass filter if V_A is input and V_B is output, and acts as a band-pass filter if V_B is input and V_A is output.



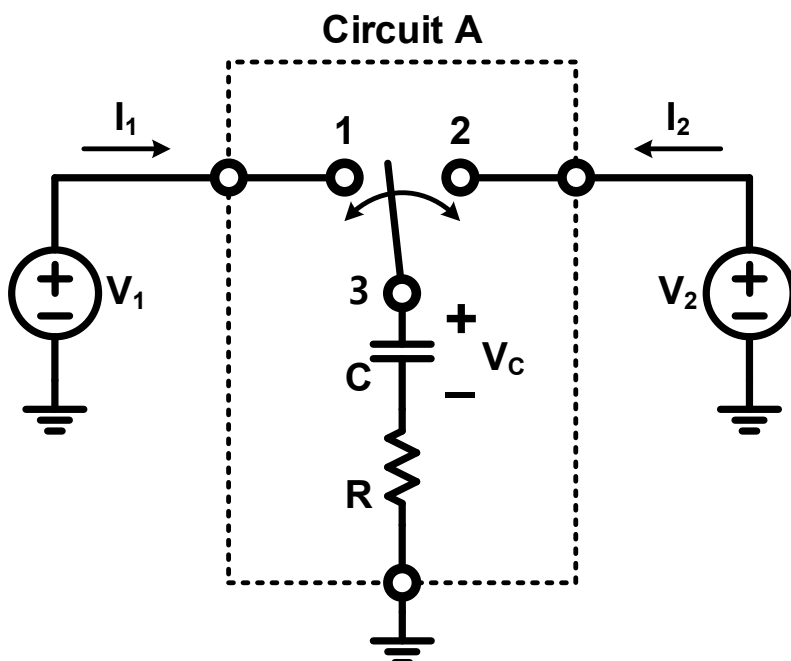Question 8. (15 points) The switch in the circuit below switches between the terminal 1 and 2 by a time period T . At $t = 0$, the switch changes the connection to connect terminals 1 and 3, and at $t = T/2$, the switch changes the connection to connect terminals 2 and 3.




Suppose V_1 and V_2 are DC voltage sources for **a) – c)**. Assume the circuit is in a periodic steady-state (all voltages and currents in the circuit are periodic with period T).

- a)** (3 points) Find the expression of V_C (voltage across C_1) for $0 \leq t \leq T$, and its rms value.
- b)** (3 points) Find the expression of I_1 and I_2 for $0 \leq t \leq T$, and their rms values.
- c)** (3 points) Find the expression of the average value of I_1 , and describe how this expression can be approximated in two extreme cases, one where $T \ll RC$ and the other where $T \gg RC$.


Suppose V_1 and V_2 are AC voltage sources with angular frequency ω for **d)** and **e)**.

- d)** (3 points) As $T \rightarrow 0$, the behavior of Circuit A converges to the behavior of a circuit without a switch. Find this circuit and justify your answer. (Hint: analyze DC and low-frequency responses assuming $T \ll RC$ and $\omega T \ll 1$.)
- e)** (3 points) Suppose $R = 10 \text{ k}\Omega$, $C = 10 \text{ nF}$, and $V_2 = 0$. Using the switch-less circuit found in **d)**, find the transfer function $G(\omega) = V_C/V_1$ and draw the Bode plot of it. Mark the position of all poles and zeros in the plot.

Question 9. The load in the circuit below draws 12kVA at $\text{pf} = 0.75$ lagging. If $|I_L| = 60 \text{ A}_{\text{rms}}$, what must be the value of C to cause the source to operate at $\text{pf} = 0.95$ lagging?

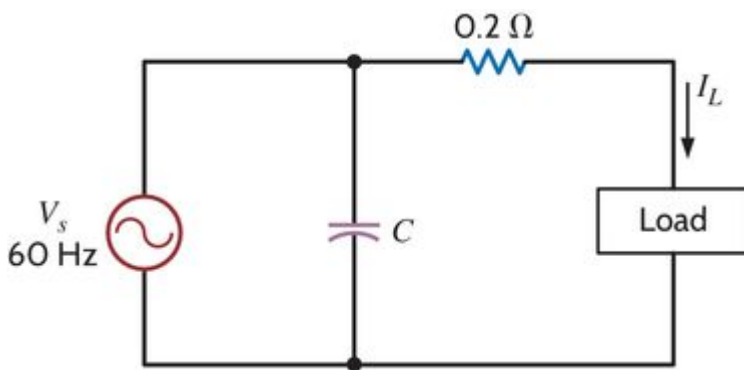


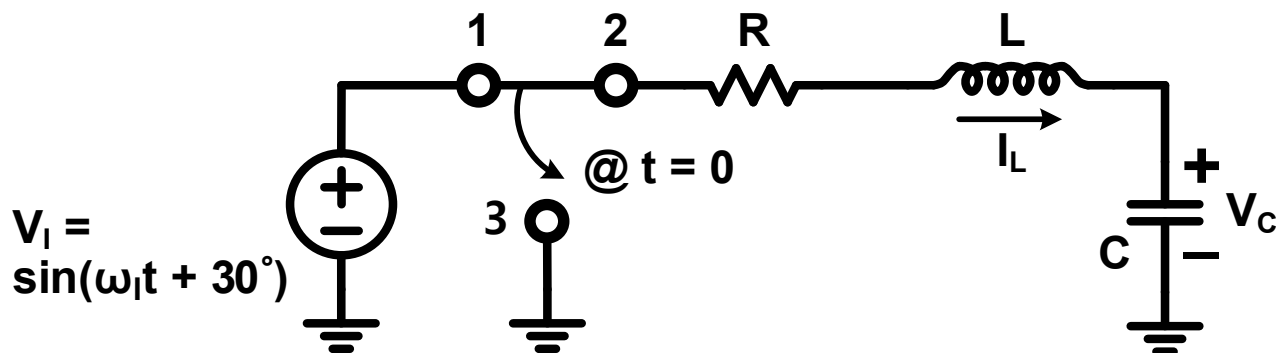Question 10. (10 points) Suppose the circuit below has been in a periodic steady-state before the switch changes connection at $t = 0$. Use $\omega_1 = 1 \text{ Mrad/s}$, $R = 2 \text{ }\Omega$, $L = 10 \text{ }\mu\text{H}$, $C = 25 \text{ nF}$



- a)** (3 points) Find the expressions of $I_L(t)$ and $V_C(t)$ for $t < 0$.
- b)** (4 points) Find the expressions of $I_L(t)$ and $V_C(t)$ for $t > 0$.
- c)** (3 points) Find the total energy stored in the capacitor and inductor at $t = 0$ and $t = \pi \text{ }\mu\text{s}$.

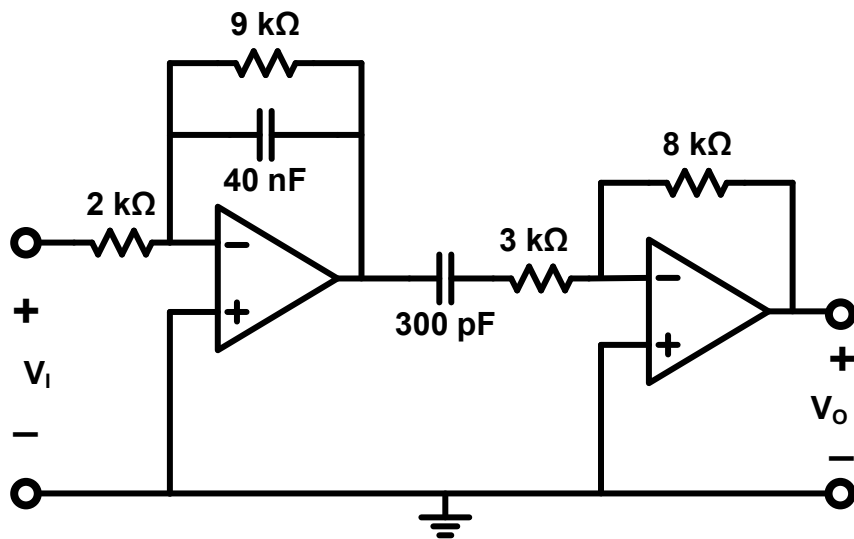Question 11. (8 points) For the circuit below,



- (4 points) Find the transfer function $G(\omega) = V_o/V_i$ and draw the Bode plot of it.
- (4 points) Find the values of ω and $G(\omega)$ where the magnitude of $G(\omega)$ is maximized.