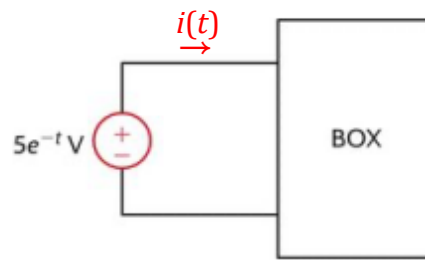


1. (6 Points) The power absorbed by the BOX in the following figure is $2e^{-2t}$ W. Calculate the amount of charge that enters the BOX between 0.1 and 0.4 seconds.



$$2e^{-2t} = 5e^{-t}i \quad 3\text{pts}$$


$$i = \frac{2e^{-2t}}{5e^{-t}} = 0.4e^{-t} \text{ A}$$

$$\begin{aligned} \Delta q(t) &= \int_{0.1}^{0.4} i(t) dt & 2\text{pts} \\ &= \int_{0.1}^{0.4} 0.4e^{-t} dt \end{aligned}$$

$$= -0.4[e^{-0.4} - e^{-0.1}] \quad 1\text{pts}$$

$$= 0.0938 \text{ C}$$

2. (6 Points) In the circuit shown below, if $V = 6\text{ V}$, find I_s .

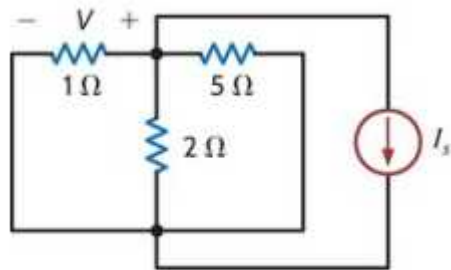

Solution 1) Calculating for each resistor

Current through $1\text{-}\Omega$ resistor: $\frac{6V}{1\Omega} = 6A$ 1pts

Current through $2\text{-}\Omega$ resistor: $\frac{6V}{2\Omega} = 3A$ 1pts

Current through $5\text{-}\Omega$ resistor: $\frac{6V}{5\Omega} = 1.2A$ 1pts

By KCL, $6A + 3A + 1.2A + I_s = 0$ 1pts

$I_s = -10.2A$ 2pts

Solution 2) Calculating for resistor in parallel

Calculation of total resistor in parallel: $1\Omega \parallel 2\Omega \parallel 5\Omega$ 1pts

$= \frac{10}{17}\Omega (= 0.588\Omega)$ 1pts


Current through total resistor in parallel: $\frac{6V}{0.588\Omega} = 10.2A$ 1pts

By KCL, $10.2A + I_s = 0$ 1pts

$I_s = -10.2A$ 2pts

-1pts for incorrect sign

3. (6 Points) In the circuit shown below, the 10-V source absorbs 2.500 mW of power. Calculate (a) V_{ba} and (b) the power absorbed by the dependent voltage source

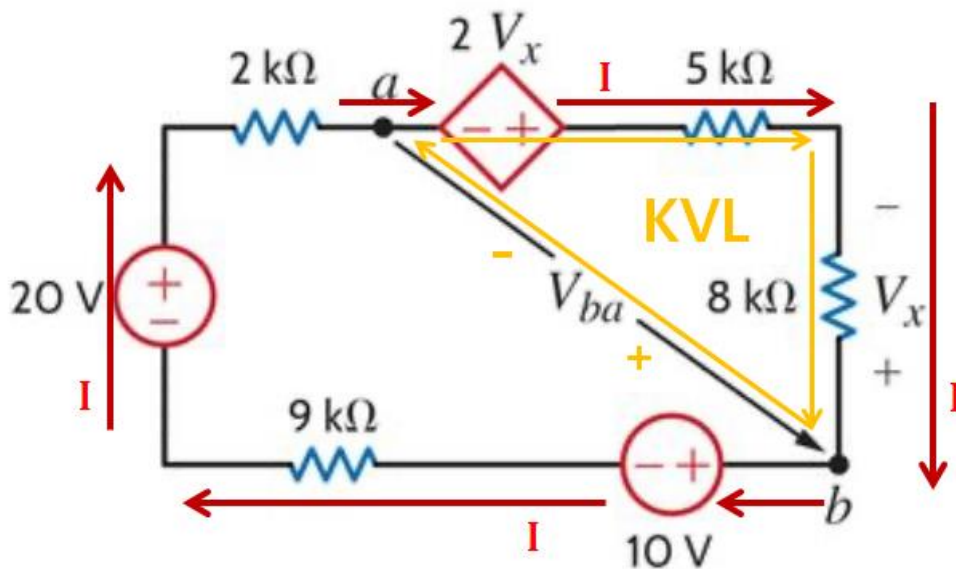

The 10-V source absorbs 2.500 mW of power :

$$P_{10V} = 2.500\text{mW (absorbed)} = 10 \cdot I$$

$$\rightarrow I = \frac{P_{10V}}{10V} = \frac{2.5\text{mW}}{10V} = 250\text{uA} \quad (\text{a}) 1.5\text{pts}$$

$$V_x = 8k \cdot (-I) = 8k \cdot (-250\text{u}) = -2\text{ V} \quad (\text{b}) 1.5\text{pts}$$

KVL :

$$\begin{aligned} V_{ba} &= V_x + 5k \cdot (-I) + 2V_x \\ &= -2 + 5k \cdot (-250\text{u}) + 2(-2) \\ &= -7.25\text{ V} \quad (\text{c}) 1.5\text{pts} \end{aligned}$$

The power absorbed by the dependent voltage source :


$$P_{2V_x} = 2V_x \cdot (-I) = 2 \cdot (-2\text{ V}) \cdot (-250\text{uA}) = 1\text{ mW} \quad (\text{d}) 1.5\text{pts}$$

In the each partial score,

-0.5pts for incorrect sign (+, -)

-0.5pts for incorrect units (A, V, W) or (m, k, u)

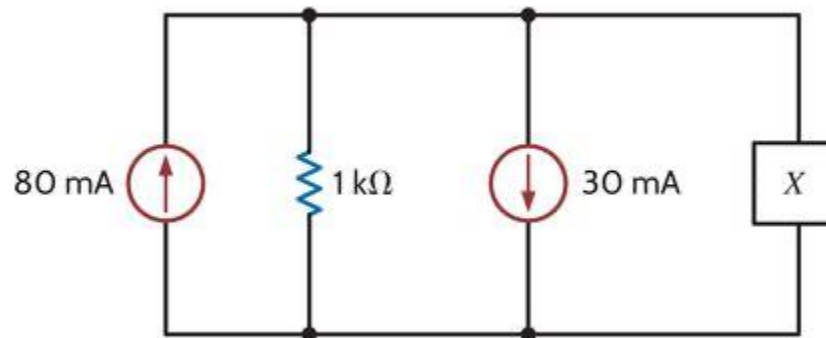4. (6 Points) (a) Let element X in the following figure be an independent current source, arrow directed upward, labeled I_s . What is I_s if none of the four circuit elements absorb any power? (b) Let element X be an independent voltage source, + reference on top, labeled V_s . What is V_s if the voltage source absorbs no power?



(a) To cancel out the effects of both the 80mA and 30 mA sources, i_s must be set to -50mA.

[+2 Points]

(b) From KCL at the top node,


$$80\text{mA} - 30\text{mA} - \frac{v_s}{1k} + i_s = 0 \quad (1) \quad [+2 \text{ Points}]$$

We are seeking a value for v_s such that $v_s \cdot i_s = 0$. (2)

Clearly, setting $v_s = 0$ will achieve this. [+1 Points]

From Eq. (1), we also see that $V_s = 50\text{V}$ will work as well. [+1 Points]

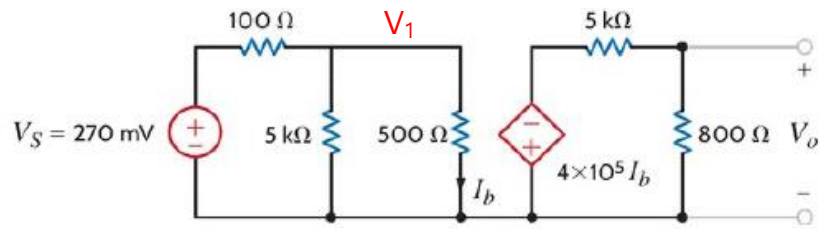5. (6 points) A typical transistor amplifier is shown below. Find the amplifier gain G (i.e., the ratio of the output voltage to the input voltage).



$$V_1 = \frac{5000 || 500}{100 + 5000 || 500} V_S = 0.221V$$

$$I_b = \frac{V_1}{500} = 442\mu A \quad 2pts$$

$$V_o = -\frac{800}{5000 + 800} (4 \times 10^5 I_b) = -24.386V \quad 2pts$$

$$G = \frac{V_o}{V_S} = -90.319 \quad 2pts$$

-0.5pts for incorrect calculation