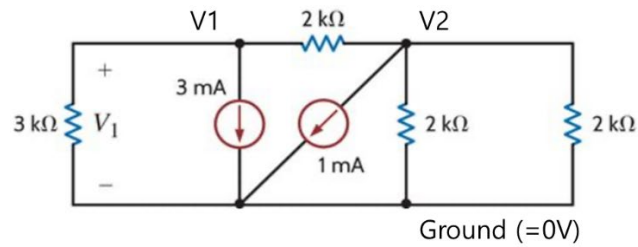


1. (6 Points) Use nodal analysis to find V_1 in the circuit shown below.



Without using nodal analysis: 0pts

Step 1

KCL @ node V1

$$\frac{V_1}{3k} + \frac{V_1 - V_2}{2k} + 3m = 0 \quad [+2]$$

KCL @ node V2

$$\frac{V_2}{2k} + \frac{V_2}{2k} + \frac{V_2 - V_1}{2k} + 1m = 0 \quad [+2]$$

Using different nodes for nodal analysis and if it is correct, you can also get full credit

Step 2

Using two equations above

$$5V_1 - 3V_2 = -18$$


$$3V_2 - V_1 = -2$$

$$V_1 = -5V$$

Answer) -5V [+2]

Wrong units (No unit) [-1]

2.

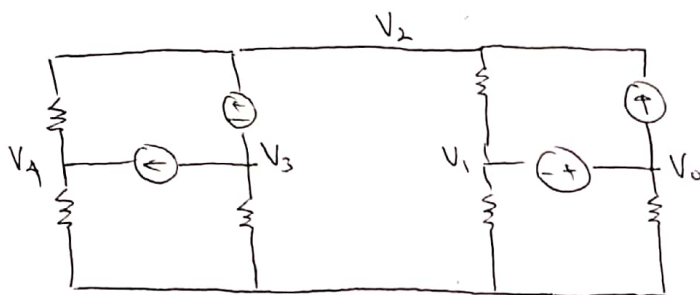

1) set five equations. less than three, deduct 1 point per each

$$V_2 - V_3 = 6 \quad \dots (1)$$

$$V_0 - V_1 = 89 \quad \dots (2)$$

~~-2V1 = 0~~

KCL @ V_2

$$\frac{V_2 - V_4}{2k} + 9m + \frac{V_3}{1k} + \frac{V_2 - V_1}{1k} - 2m = 0 \quad \dots (3)$$

KCL @ $V_1 \sim V_0$

$$\frac{V_1}{1k} + \frac{V_1 - V_2}{1k} + 2m + \frac{V_0}{1k} = 0 \quad \dots (4)$$


KCL @ V_4

$$9m = \frac{V_4}{2k} + \frac{V_4 - V_2}{2k} \quad \dots (5)$$

2) answer. 3 points. ± 1 error allowed.

$$V_0 = 54 (V)$$

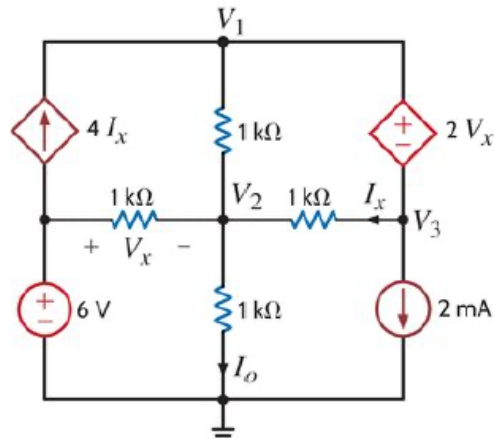3. (6 Points) Use nodal analysis to find I_o in the circuit shown below.



To find V_1 , V_2 , V_3 , V_x and I_x , we have to find out 5 equations.

$$\frac{V_1 - V_2}{1k} + \frac{V_3 - V_2}{1k} - 4I_x = -\frac{2}{1k} \quad \dots (1) \quad 1 \text{ pt}$$

$$I_x = \frac{V_3 - V_2}{1k} \quad \dots (2) \quad 1 \text{ pt}$$

$$V_1 - V_3 = 2V_x \quad \dots (3) \quad 1 \text{ pt}$$

$$V_x = 6 - V_2 \quad \dots (4) \quad 1 \text{ pt}$$

$$\frac{V_2 - 6}{1k} + \frac{V_2 - V_1}{1k} + \frac{V_2 - V_3}{1k} + \frac{V_2}{1k} = 0 \quad \dots (5) \quad 1 \text{ pt}$$

From (1) and (2),

$$V_1 + 2V_2 - V_3 = 12 \quad \dots (6)$$

From (2), (3), and (4)

$$V_1 + 2V_2 - V_3 = 12 \quad \dots (7)$$

From (5),

$$-V_1 + 4V_2 - V_3 = 6 \quad \dots (8)$$

From (6), (7), and (8)

$$V_2 = \frac{16}{3} \text{ V}$$

$$I_o = \frac{V_2}{1k} = \frac{16}{3} \text{ mA} \quad 1 \text{ pt}$$

3.65 Determine each mesh current in the circuit in Fig. P3.65.

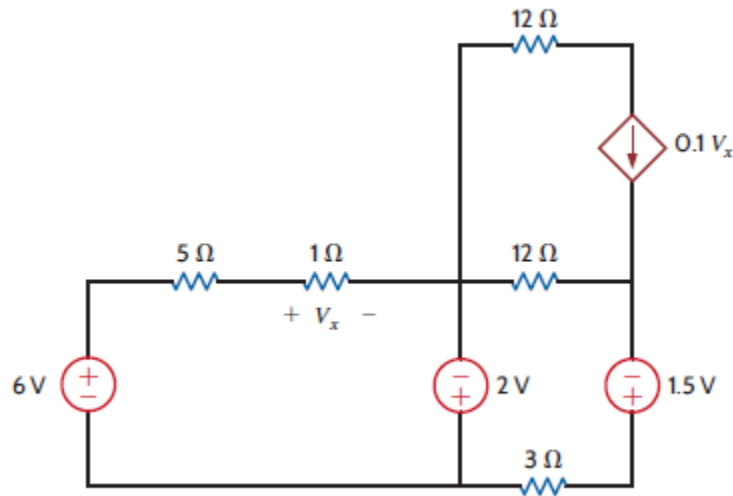


Figure P3.65

SOLUTION:

We define a clockwise mesh current i_3 in the upper right mesh, a clockwise mesh current i_1 in the lower left mesh, and a clockwise mesh current i_2 in the lower right mesh.

$$\text{MESH 1: } -6 + 6i_1 - 2 = 0 \quad | \quad [1]$$

$$\text{MESH 2: } 2 + 15i_2 - 12i_3 - 1.5 = 0 \quad | \quad [2]$$

$$\text{MESH 3: } i_3 = 0.1v_x \quad | \quad [3]$$

Eq. [1] may be solved directly to obtain $i_1 = 1.333 \text{ A}$. $|$

It would help in the solution of Eqs. [2] and [3] if we could express the dependent source controlling variable v_x in terms of mesh currents. Referring to the circuit diagram, we see

that $v = (1)(i_1) = i_1$, so Eq. [3] reduces to

$$i_3 = 0.1v_x = 0.1i_1 = 133.3 \text{ mA} \quad |$$


As a result, Eq. [1] reduces to

$$i_2 = [-0.5 + 12(0.1333)] / 15 = 73.31 \text{ mA} \quad |$$

[채점기준]

- Each expression of mesh 1, 2, 3 is correct : 1pts for each 3pts
- Each mesh current i_1, i_2, i_3 is correct : 1pts for each 3pts
- Total 6pts

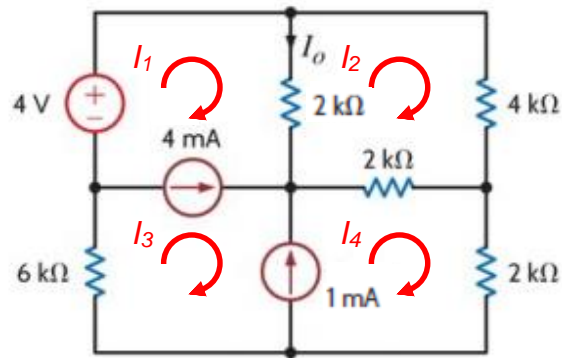5. (6 points) Find I_o in the circuit shown below using loop analysis.



$$I_3 - I_1 = 4 \text{ mA} \dots\dots (i) \quad 1\text{pts}$$

$$I_4 - I_3 = 1 \text{ mA} \dots\dots (ii) \quad 1\text{pts}$$

$$2k(I_2 - I_1) + 4kI_2 + 2k(I_2 - I_4) = 0$$

$$4I_2 - I_1 - I_4 = 0 \dots\dots (iii) \quad 1\text{pts}$$

$$4 - 4kI_2 - 2kI_4 - 6kI_3 = 0 \dots\dots (iv) \quad 1\text{pts}$$

$$\text{By (iii), (iv), } -4m + I_1 + 3I_4 + 6I_3 = 0 \dots\dots (v)$$

$$\text{By (i), (ii), (v), } -4m + (I_3 - 4m) + 3(I_3 + 1m) + 6I_3 = 0$$

$$I_3 = 0.5 \text{ mA}$$

$$\therefore I_1 = 0.5 \text{ m} - 4m = -3.5 \text{ mA}, I_4 = 1.5 \text{ mA}, I_2 = -0.5 \text{ mA}$$

$$\therefore I_o = I_1 - I_2 = -3 \text{ mA} \quad 2\text{pts}$$