

ID:  
NAME:

EE201 Circuit Theory  
KAIST, Fall 2013

Oct. 16, 2013

---


### Quiz #1 [50pts]

---

#### Problem Sets

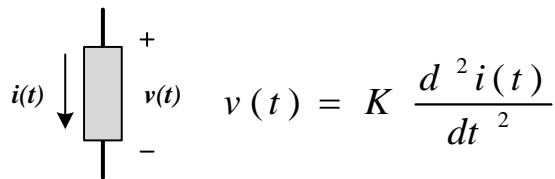1. If the input and output is current and voltage, is the following element linear? [5pts]

Ans: (Yes, No, Depends on situation) (3 points deducted if incorrect. No need to provide proof.)




Sol)

Yes.

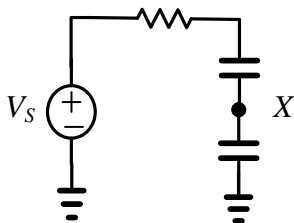2. Is it possible for the net charge on node X to change if you can provide ANY voltage source at the input  $V_s$ ?


Ans: (Yes, No, Depends on the input) (3 points deducted if incorrect, No need to provide any explanation.)  
[5pts]



Sol)

No.

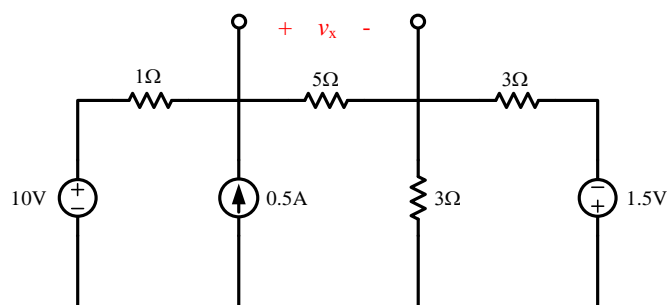
3. Determine the Thévenin equivalent of the network shown as below as seen looking into  $v_x$ . [10pts]



ID:  
NAME:

Sol)
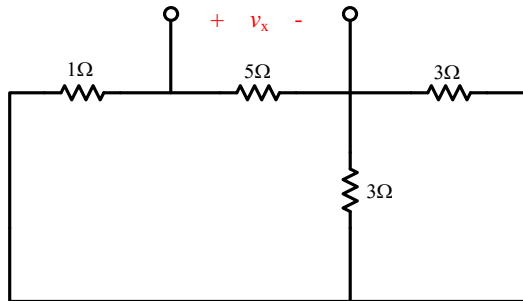
$$R_{th} = 5 \parallel (1 + 3 \parallel 3) = \frac{5}{3} \Omega$$





Use KCL

$$\frac{v_1 - 10}{1} - 0.5 + \frac{v_1 - v_2}{5} = 0$$


$$\frac{v_2 - v_1}{5} + \frac{v_2}{3} + \frac{v_2 - (-1.5)}{3} = 0$$
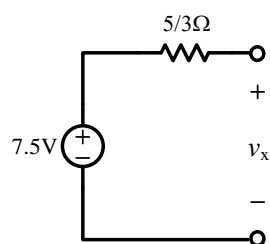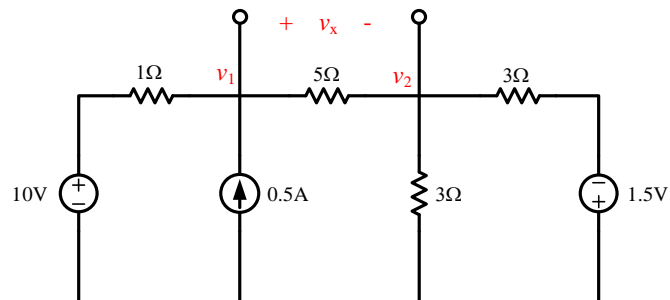
$$v_1 = 9V, \quad v_2 = 1.5V, \quad v_x = 7.5V$$



ID:  
NAME:

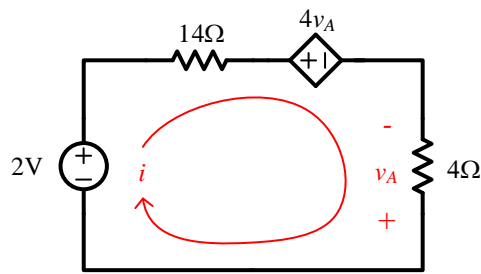4. What is the power absorbed by the 4 ohm resistor in the circuit shown below? [10pts]



Sol)

Use KVL


$$-2 + 14i + 4v_A + 4i = 0, \quad i = \frac{-v_A}{4}$$

$$-2 + 14i + 4 \times (-4i) + 4i = -2 + 14i - 16i + 4i = 2 + 2i = 0$$


$$i = 1A$$

$$P = I^2 R = 1^2 \times 4 = 4W$$

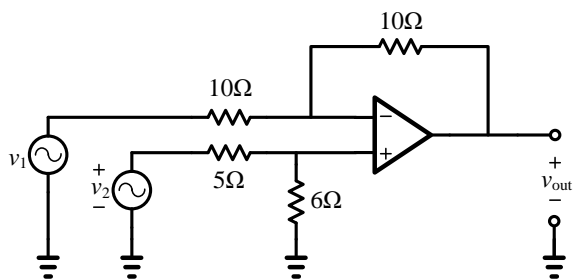5. Derive an expression for  $v_{out}$  as a function of  $v_1$  and  $v_2$  for the circuit represented as below. [10pts]



Sol)

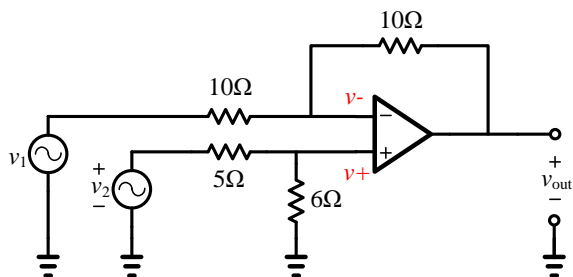

$$v_+ = v_- = \frac{6}{5+6} v_2 = \frac{6}{11} v_2$$


$$\frac{v_- - v_1}{10} + \frac{v_- - v_{out}}{10} = 0, \quad 2v_- - v_1 - v_{out} = 0$$

$$v_{out} = 2v_- - v_1 = \frac{12}{11} v_2 - v_1$$

ID:


NAME:

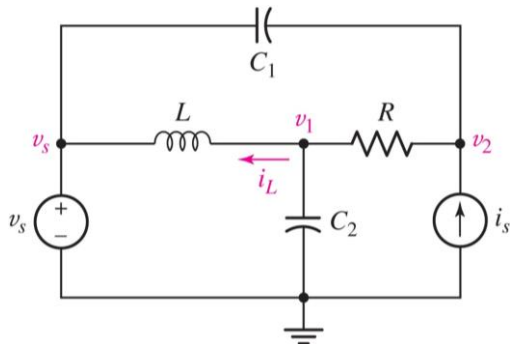6. Find the final steady-state output voltage of  $v_1$  and  $v_2$  in the below circuit. Assume  $v_s = 2V$ ,  $i_s = 2A$ ,  $R = 2\Omega$ ,  $L = 1nH$ ,  $C_1 = 1\mu F$ ,  $C_2 = 5\mu F$ . Assume initial conditions of all elements are zero. [10pts]



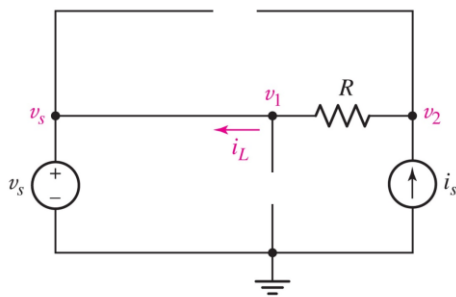**Sol)**

At final steady-state, capacitor acts as a open circuit. Inductor acts as a short circuit.



$$v_s = v_1 = 2V$$

$$v_2 - v_1 = R \times i_s = 2 \times 2 = 4V$$

$$v_1 = 2V, \quad v_2 = 6V$$