

EE201 Circuit Theory (Fall 2020)

Final Exam.


(Total: 240 Points / 8 Problems)

Student ID Number:


Name:

Prob. 1	Prob. 2	Prob. 3	Prob. 4	Prob. 5	Prob. 6	Prob. 7	Prob. 8	Total
/30	/30	/30	/30	/20	/30	/40	/30	/240

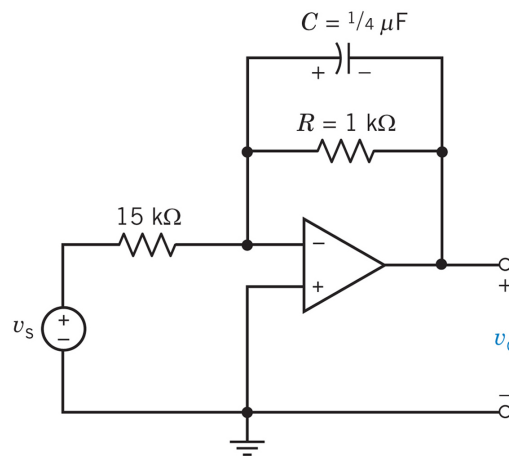1. **(30 points) Response of a First-Order Circuit to a Nonconstant Source:** A lossy integrator is shown below. The lossless capacitor of the ideal integrator circuit has been replaced with a model for the lossy capacitor, namely, a lossless capacitor in parallel with a 1-k Ω resistor. If $v_s(t) = 8e^{-5t}u(t)$ V and $v_o(0) = 10$ V, find $v_o(t)$ for $t > 0$. Assume that the circuit is at steady state before $t = 0$.




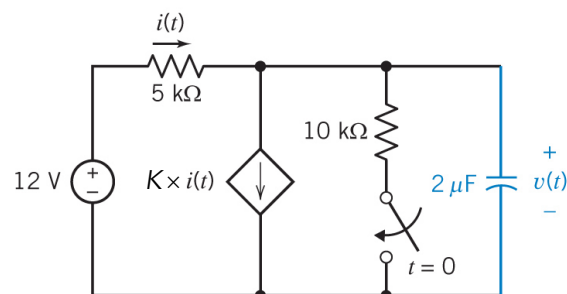2. **(30 points) Stability of First-Order Circuits:** The first order circuit shown below is at steady state before the switch closes at $t = 0$. This circuit contains a dependent source and so may be unstable. K is a gain of the dependent source.




- (a) **(5 points)** Find the initial capacitor voltage at $t = 0$, which is $v(0)$.
- (b) **(10 points)** Determine the Thevenin equivalent for the entire circuit except the capacitor.
- (c) **(10 points)** For $K = 2$, find the capacitor voltage $v(t)$ for $t > 0$. What is the value of $v(t)$ at $t = \infty$, which is $v(\infty)$? Is this circuit stable?
- (d) **(5 points)** What restriction must be placed on K to ensure that the circuit is stable?

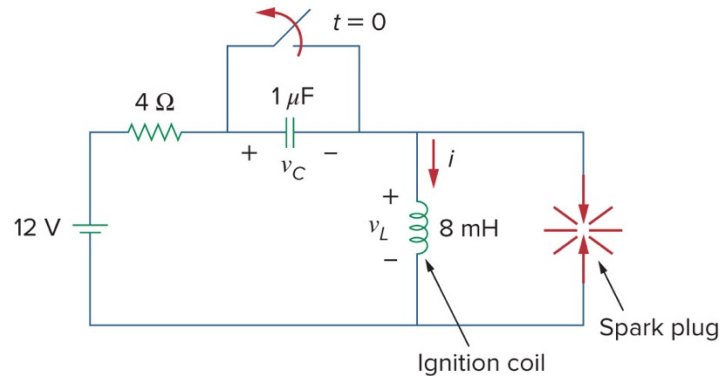
3. **(30 points) Automobile Ignition System:** The automobile ignition system is modeled by the circuit shown below. The 12-V source represents the battery, and the 4- Ω resistor models the resistance of the wiring. The ignition coil is modeled by the 8-mH inductor. The 1- μ F capacitor is in parallel with the switch.



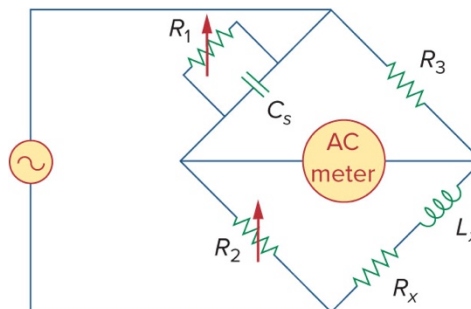
- (a) **(20 points)** Assuming that the switch is closed prior to $t = 0$, find the inductor voltage $v_L(t)$ for $t > 0$.
- (b) **(5 points)** Find the maximum value of $v_L(t)$.
- (c) **(5 points)** Find the capacitor voltage $v_C(t)$ for $t > 0$.
4. **(30 points) AC Bridge Circuits:** Answer the following questions.
- (a) **(15 points)** The AC bridge circuit shown below is known as a Maxwell bridge and is used for accurate measurement of inductance L_x and resistance R_x of a coil in terms of a standard capacitance C_s . Show that when the bridge is balanced (= when zero current flows through the AC meter), $L_x = R_2 R_3 C_s$ and $R_x = (R_2/R_1)R_3$.



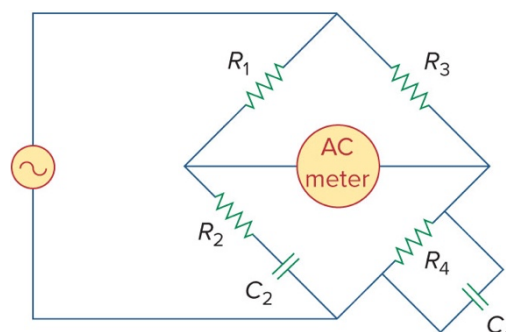
- (b) **(15 points)** The AC bridge circuit shown below is called a Wien bridge. It is used for measuring the frequency of an AC source. Show that when the bridge is balanced, $f = 1/[2\pi(R_2 R_4 C_2 C_4)^{0.5}]$.



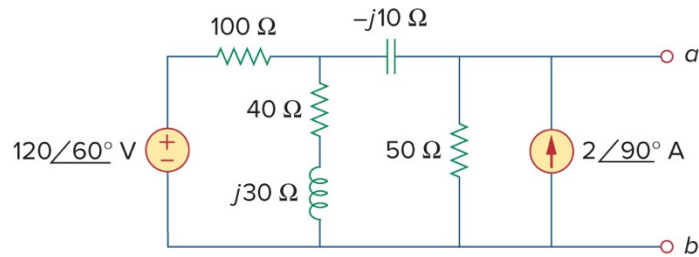5. **(20 points) Maximum Average Power Transfer:** Assuming that the load impedance is to be purely resistive, what load should be connected to terminals a – b of the circuit shown below so that the maximum average power is transferred to the load?



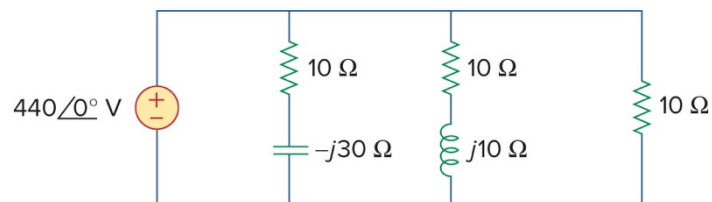
6. **(30 points) Power Factor Correction:** For the power system shown below, answer the following questions. Note that the voltage is in RMS value.




- (a) **(15 points)** Find the total complex power delivered to the entire parallel combination of loads.
- (b) **(5 points)** Calculate the power factor of the entire parallel combination of loads.
- (c) **(10 points)** Find the value of the parallel capacitance necessary to establish a unity power factor.

7. (40 points) Filter Circuits: Answer the following questions.

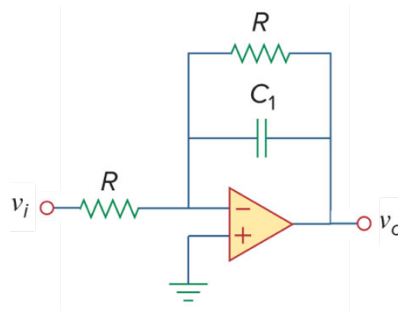
(a) (10 points) Find the transfer function $H_1(\omega) = V_o/V_i$ of the circuit shown below. Which type of filter is it? What is the value of the cutoff frequency ω_1 ?



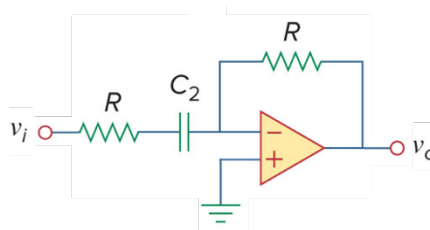(b) (10 points) Find the transfer function $H_2(\omega) = V_o/V_i$ of the circuit shown below. Which type of filter is it? What is the value of the cutoff frequency ω_2 ?



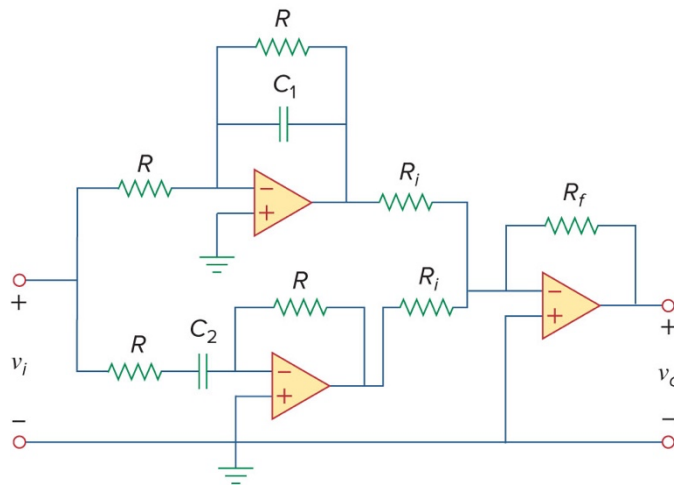(c) (10 points) Express the transfer function $H(\omega) = V_o/V_i$ of the following circuit in terms of ω_1 and ω_2 . Which type of filter is it, if ω_1 is smaller than ω_2 ?



(d) (10 points) In (c), find the gain at $\omega = 0$ and ∞ . Also find the gain at the center frequency $\omega_0 = (\omega_1\omega_2)^{0.5}$.

8. **(30 points) Bode Plot of a Circuit:** Consider the circuit shown below. The network function that represents this circuit is $H(\omega) = V_o/V_i$ and the corresponding magnitude plot is also shown below. Determine the values of the capacitances C_1 and C_2 .

