

Mid-Term Exam (3 hours)

1. [Linearity & Electrical elements] [12pts]


- (a) Suppose the input and the output of a resistor are defined as voltage across the device and temperature of the device, respectively. Is this system linear? Assume that the temperature is proportional to power dissipated in the resistor. [2pts]

Sol)


No, it isn't.

$$T \propto P = \frac{V^2}{R}$$

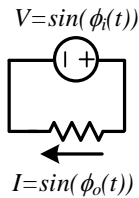- (b) Suppose the input and output of the below circuits are the phase of the voltage and current, respectively. (i.e., input = $\phi_i(t)$, output = $\phi_o(t)$) Is this system linear? Assume $R=1\Omega$, $C=1F$. [4pts]



Linear? (**Yes**, No)

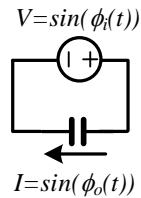

Linear? (Yes, **No**)

Sol)

Resistor

$$V = RI = I$$

$$\sin(\phi_i(t)) = \sin(\phi_o(t))$$

$$\phi_i(t) = \phi_o(t)$$

Capacitor






$$I = C \frac{dV}{dt} = \frac{dV}{dt}$$

$$\sin(\phi_i(t)) = \frac{d \sin(\phi_o(t))}{dt} = \phi_o'(t) \cos(\phi_o(t))$$






$\phi_o(t)$ and $\phi_i(t)$ are not in linear relationship.

학번(ID): _____ 이름(Name): _____

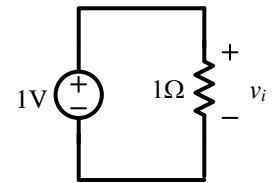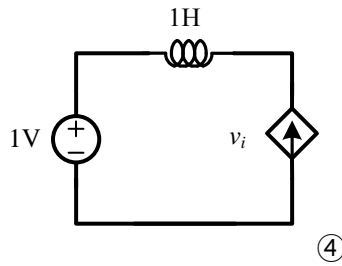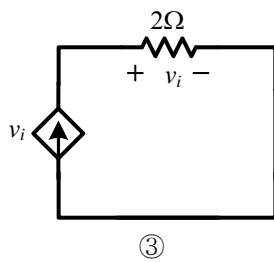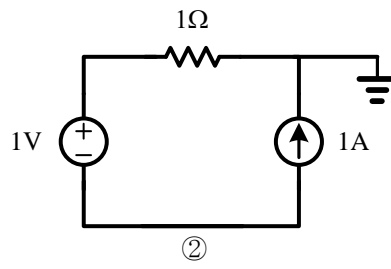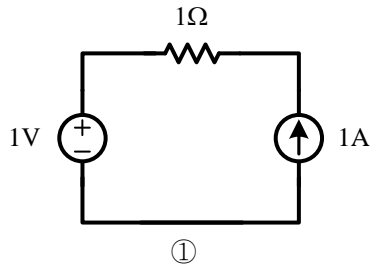(c) Please choose the circuits that are physically possible ($0 < v_i < \infty$). [6pts]



Sol)

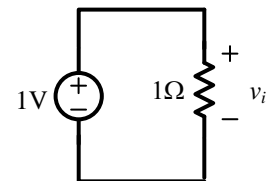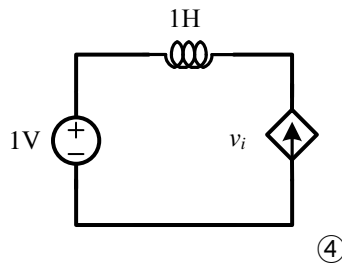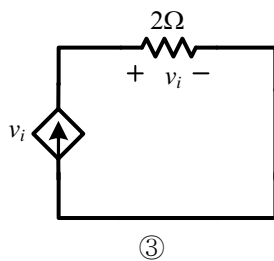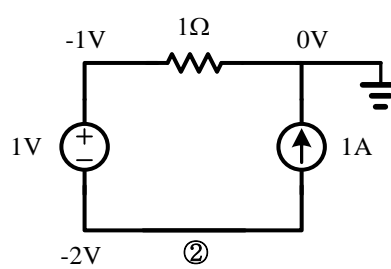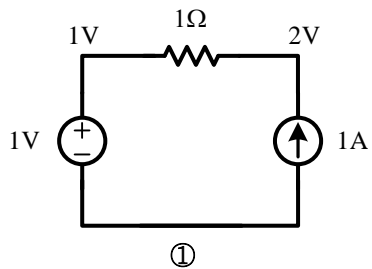

① See above figure


② See above figure

③ $v_i = 2v_i$, $v_i = 0$

④ $v_i = 1V$

Answer: (①, ②, ④)

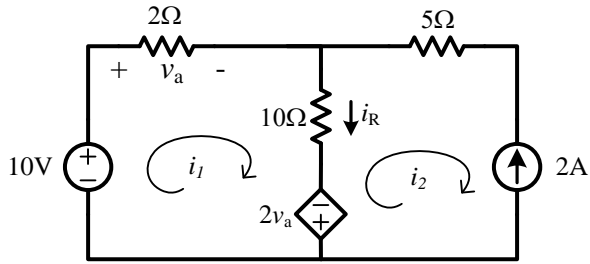2. Analyze the circuit shown below. [9pts]



- (a) Write down two equations necessary to analyze this circuit. [6pts]

Sol)

$$-10 + 2i_1 + 10(i_1 - i_2) - 2 \cdot 2i_1 = 0$$


$$i_2 = -2A$$

- (b) Find i_R and the mesh currents i_1 and i_2 . [3pts]

Sol)


From (a), $i_1 = -1.25A$, $i_2 = -2A$. Thus, $i_R = 0.75A$.

3. [Thevenin & Norton] [8pts]

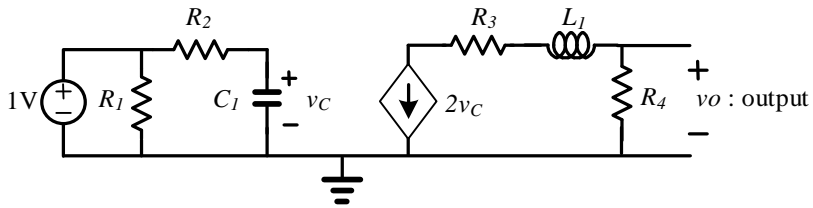

- (a) Find the Thevenin equivalent of the above circuit seen from the output at DC. [5pts]


Sol)

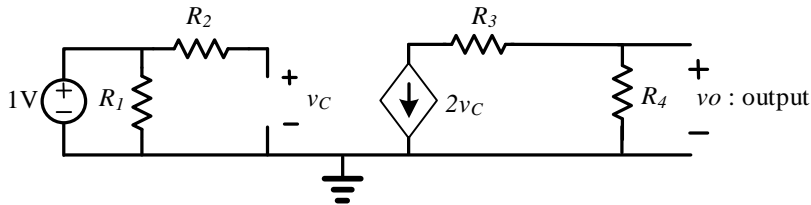



$$v_c = 1V$$

$$v_o = v_{th} = -2v_c R_4 = -2R_4$$

$$R_{th} = R_4$$

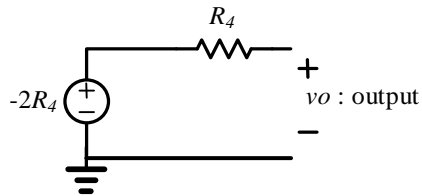

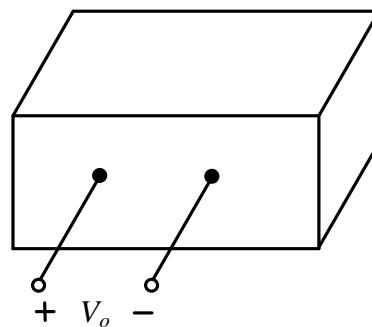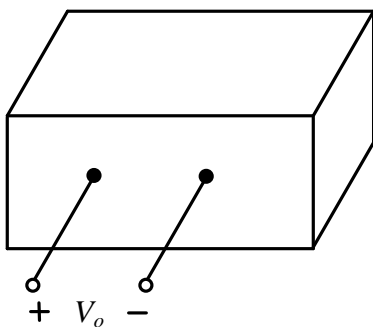- (b) Suppose there are two boxes with two electrical outputs. One has a Thevenin equivalent circuit of the above circuit, and the other has the Norton equivalent. Please describe how you can distinguish Norton and Thevenin between these two boxes. [3pts]



Sol)


Solution 1

It cannot be distinguished electrically.

Solution 2

It can be distinguished by measuring temperature when the output is open since current always flows in the Norton equivalent circuit.

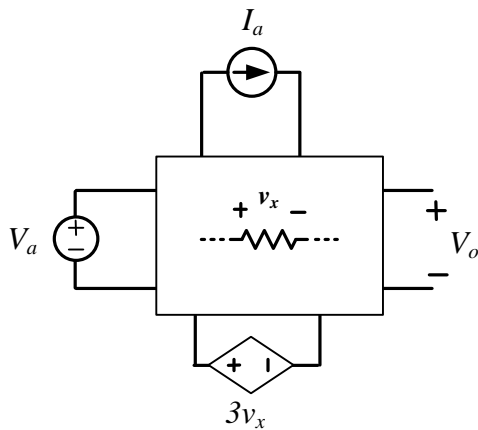4. Please consider the circuit shown below. The rectangular box consists of resistors, capacitors and inductors only. Note that a dependent source is affected by one of the resistor in the box. [9pts]



- (a) Suppose that $V_o = 0.5V$ when $(V_a, I_a) = (2V, 3A)$ and $V_o = 1V$ when $(V_a, I_a) = (3V, 4A)$, respectively. What is the value of V_o when $(V_a, I_a) = (1V, 2A)$? If it is not solvable, explain why. [5pts]

Sol)

This system is linear, so the independent variables can form a linear combination.

$$V_o = a_1 \cdot V_a + a_2 \cdot I_a$$

Using superposition principle, we can manipulate above equation with the given conditions to get a_1 and a_2 which are 1 and -0.5, respectively.

$$\therefore V_o = 1 \cdot 1 - 0.5 \cdot 2 = 0$$


- (b) Suppose the dependent source is changed to $3v_x^2$. Repeat (a). If it is not solvable, explain why. [4pts]

Sol)

With the dependent source, it is not solvable with given condition because this system is not linear.

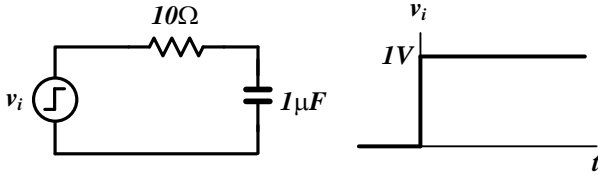5. Please consider the circuit shown below. Assume that the circuit reaches steady-state when calculating energy. [12pts]

For (a) ~ (c), consider the circuit shown below. Assume that the initial charge in the capacitor is zero.



- (a) What is the energy stored in the capacitor? [2pts]

Sol)

$$v_c(t) = \Delta v_i \left(1 - e^{-\frac{t}{RC}}\right) + v_c(0^+), i(t) = \frac{\Delta v_i}{R} e^{-\frac{t}{RC}} \text{ and } v_c(0^+) = 0V.$$

$$E_C = \frac{1}{2} C v_c^2(\infty) = 0.5 \mu J$$

- (b) What is the energy drawn from the source? [2pts]

Sol)

$$E_V = \int_0^\infty p(t) dt = \int_0^\infty v_i(t) \cdot i(t) dt = v_i(0^+) \int_0^\infty i(t) dt = \frac{\Delta v_i^2}{R} \int_0^\infty e^{-\frac{t}{RC}} dt = C \Delta v_i^2 = 1 \mu J$$

- (c) What is the energy absorbed (dissipated) in the resistor? [2pts]

Sol.1)


$$E_R = E_V - E_C = 0.5 \mu J$$

Sol.2)

$$v_R(t) = v_i(t) - v_c(t) = \Delta v_i - \Delta v_i \left(1 - e^{-\frac{t}{RC}}\right) = \Delta v_i \cdot e^{-\frac{t}{RC}}$$

$$E_R = \int_0^\infty p(t) dt = \int_0^\infty v_R(t) \cdot i(t) dt = \frac{\Delta v_i^2}{R} \int_0^\infty e^{-\frac{2t}{RC}} dt = \frac{1}{2} C \Delta v_i^2 = 0.5 \mu J$$

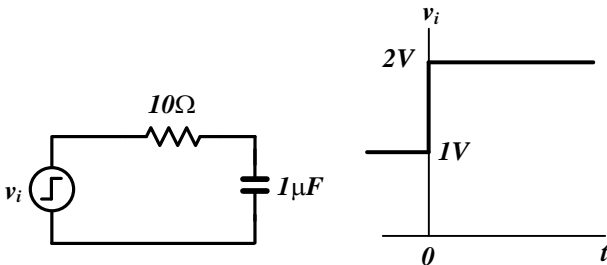For (d) ~ (e), consider the circuit shown below. Assume that the initial voltage across the capacitor is 1V.



- (d) What is the energy stored in the capacitor? [2pts]

Sol)

$$v_c(t) = \Delta v_i \left(1 - e^{-\frac{t}{RC}}\right) + v_c(0^+), i(t) = \frac{\Delta v_i}{R} e^{-\frac{t}{RC}} \text{ and } v_c(0^+) = 1V.$$

$$E_C = \frac{1}{2} C v_c^2(\infty) = 2 \mu J.$$

학번(ID): _____ 이름(Name): _____

- (e) What is the energy drawn from the source? [2pts]

Sol)

$$E_V = \int_0^{\infty} p(t) dt = v_i(0^+) \int_0^{\infty} i(t) dt = \frac{v_i(0^+) \cdot \Delta v_i}{R} \int_0^{\infty} e^{-\frac{t}{RC}} dt = C v_i(0^+) \cdot \Delta v_i = 2 \mu J$$

- (f) What is the energy absorbed (dissipated) in the resistor? [2pts]


Sol)

$$v_R(t) = v_i(t) - v_C(t) = v_i(0^+) - \left[v_C(0^+) + \Delta v_i \left(1 - e^{-\frac{t}{RC}} \right) \right] = e^{-\frac{t}{RC}}$$

$$E_R = \int_0^{\infty} p(t) dt = \int_0^{\infty} i(t) \cdot v_R(t) dt = \frac{1}{R} \int_0^{\infty} e^{-\frac{2t}{RC}} dt = \frac{1}{2} C = 0.5 \mu J$$

6. [Opamp and Feedback] [13pts]

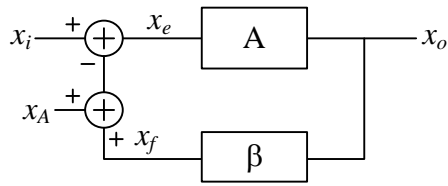(a) Consider the block diagram below. [3pts]



i. Express x_e in terms of x_i , x_A , A and β . [2pts]

Sol)


$$\begin{aligned} x_e &= x_i - (x_A + x_f) \\ &= x_i - (x_A + \beta x_o) \\ &= x_i - (x_A + A\beta x_e) \\ \Rightarrow x_e &= (x_i - x_A) / (1 + A\beta) \end{aligned}$$

ii. What happens to x_e as A goes to infinity? [1pt]

Sol)

x_e goes to zero.

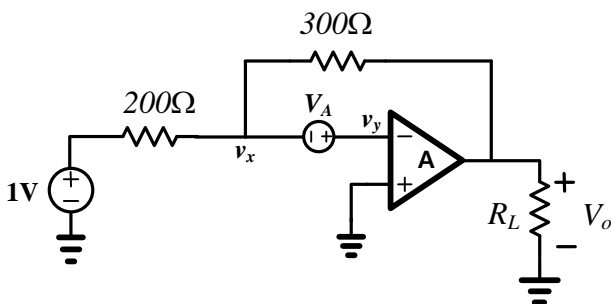For (b) ~ (e), consider the circuit shown below. Assume that the opamp is ideal. (i.e. $A = \infty$)



(b) Suppose $V_A=0$ and $R_L = 100\Omega$. What is V_o ? [3pts]

Sol)

$$V_o = \left(-\frac{300\Omega}{200\Omega} \right) \cdot 1V = -1.5V.$$

(c) Suppose $V_A \neq 0$ and $R_L = 100\Omega$. [5pts]

i. Which of the following is true? [2pts]

① $v_x=0$ ② $v_y=0$ ③ none of the above.

ii. Express V_o in terms of V_A . [3pts]


Sol)

$$\begin{aligned} \frac{-V_A - 1}{200} &= \frac{V_o + V_A}{300} \\ \Rightarrow V_o &= -V_A \left(1 + \frac{3}{2} \right) - \frac{3}{2} \end{aligned}$$


(d) What is the value of R_L that results in maximum power transfer? Assume $V_A = 0$. [2pts]

① 200Ω ② 300Ω ③ 120Ω ④ 500Ω ⑤ **There is no specific value that results in maximum power transfer.**


7. [RC Circuit] [16pts]

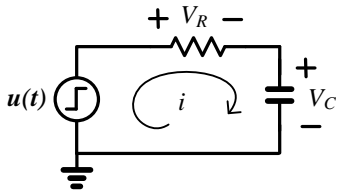

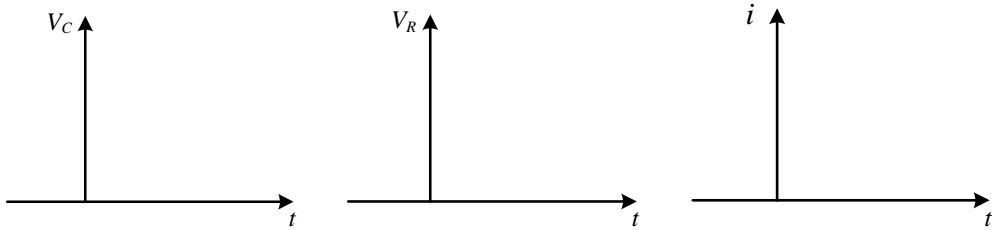
- (a) Draw the voltage V_C , V_R and the current i when step input is applied for the above circuit. Assume that the initial charge in the capacitor is zero. Draw the answer both when $t > 0$ and $t < 0$. [6pts]




Sol)

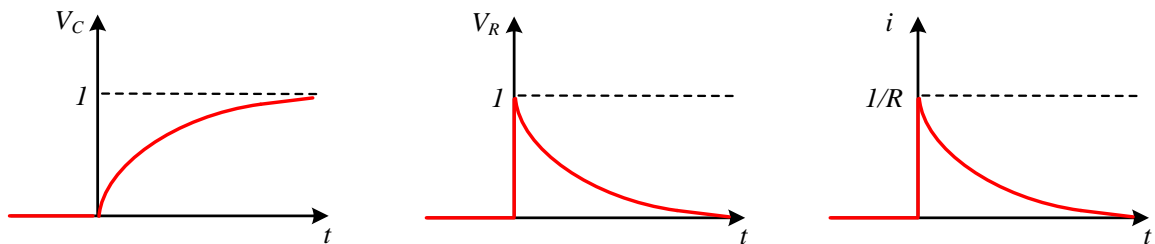

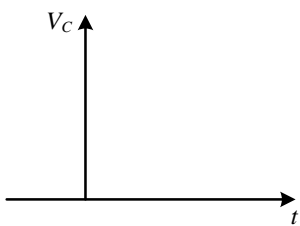- (b) Suppose the initial charge is $0.5V$. Draw the answer when $t > 0$ [2pts]




Sol)

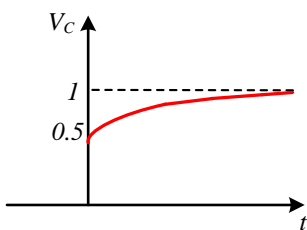


학번(ID): _____ 이름(Name): _____

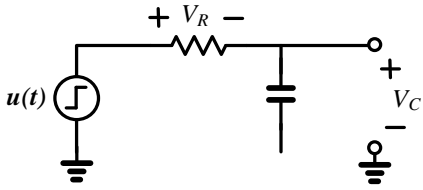
Suppose the circuit is cut and the ground is removed from the capacitor, as shown below.



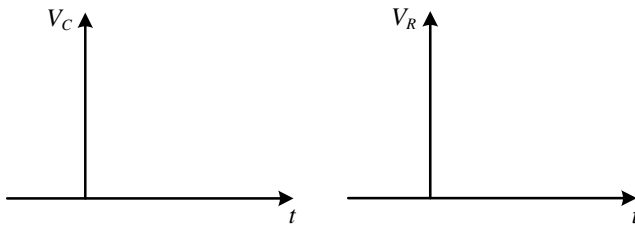
(c) Repeat (a) for the circuit shown in right. [6pts]




Sol)

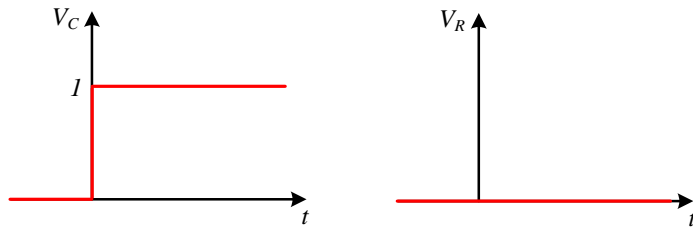

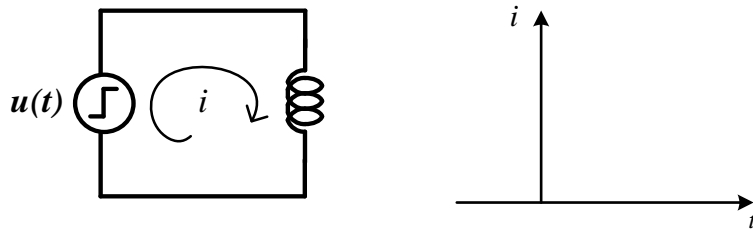
(d) Draw the output current i in the below figure. Assume that initial current is zero. [2pts]




Sol)

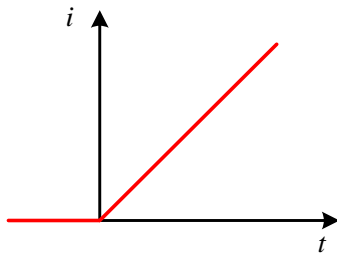

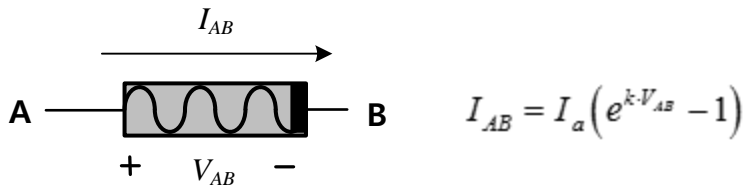8. Consider the following 2-terminal device which has the following characteristics. [13pts]



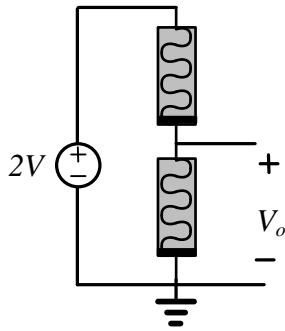- (a) What is the output voltage, V_O , of the below circuit? Assume $I_a = 10^{-6}$ (A) and $k = 0.5$ (V⁻¹) [3pts]




Sol)

The amount of current that flows through two elements is the same, so the voltage drop across the two elements should be the same.

$$\therefore V_O = \frac{2V}{2} = 1V$$

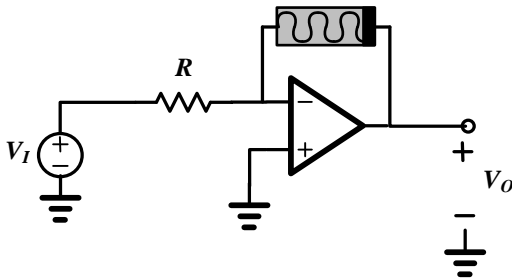- (b) Analyze the circuit shown below. Assume that the opamp is ideal. [5pts]



- i. Is the circuit in a positive feedback or negative feedback? If the circuit does not operate properly, please fix the circuit so that it is stable. [1pt]

Sol)

It is a negative feedback. It operates properly.

- ii. Write down the equation for KCL. Express your answer in terms of V_O , V_I , R , k and I_a . [2pts]

Sol)

$$\frac{0 - V_I}{R} + I_{AB} = -\frac{V_I}{R} + I_a (e^{k(0 - V_O)} - 1) = 0 \rightarrow -\frac{V_I}{R} + I_a (e^{k(-V_O)} - 1) = 0$$

- iii. Express V_O in terms of V_I , R , k and I_a . [2pts]

Sol)


$$e^{k(-V_O)} = \frac{V_I}{R \cdot I_a} + 1$$

$$V_O = -\frac{1}{k} \ln \left(\frac{V_I}{R \cdot I_a} + 1 \right)$$

학번(ID): _____ 이름(Name): _____

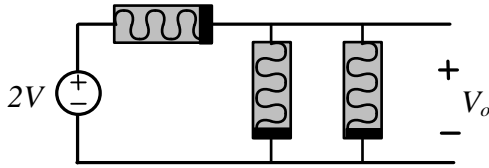
- (c) What is the approximate output voltage, V_o ? In order to calculate the approximate V_o , please assume that $I_{AB} \cong I_a e^{k \cdot V_{AB}}$.

Assume $I_a = 10^{-6}$ (A) and $k = 0.5$ (V⁻¹) [5pts]



Sol)

Using KCL,

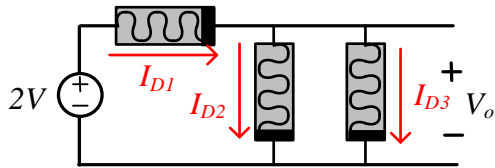

$$I_{D2} = I_{D3}$$

$$I_{D1} = I_{D2} + I_{D3} = 2I_{D2}$$


$$I_a e^{k \cdot (2 - V_o)} = 2I_a e^{k \cdot V_o}$$

$$k \cdot (2 - V_o) = k \cdot V_o + \ln 2$$

$$2V_o = 2 - \frac{\ln 2}{k} = 2 - \frac{\ln 2}{0.5}$$

$$V_o = 1 - \ln 2$$

9. [RC Circuit] [8pts]

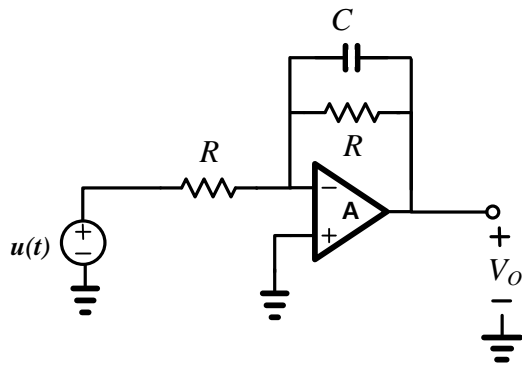

- (a) What is the time-constant of the above circuit? [3pts]

Sol)

Resistance seen from the two terminals of the capacitor is R . Thus, $\tau = RC$.

- (b) Draw a circuit that exhibits the same output voltage as the above circuit using a capacitor, a resistor, and a unit-step voltage source. [5pts]

Sol)

