

EE303A Digital System Design

Midterm

9:00 AM - **11:45** AM, April 21st, 2022

ID:

Name:

	Prob. 1	Prob. 2	Prob. 3	Prob. 4	Prob. 5	Total
Score	/80	/20	/30	/20	/30	/180

Read carefully before starting exam:

- ❖ You must stay until the exam is complete.
 - ✓ Write your answer **from 9:00 AM - 11:30 AM**. Do not touch your phone during this time.
 - ✓ Photograph and submit your answer **from 11:30 AM to 11:45 AM**. Do not write anything on your answer sheet during this time.
 - ✓ You must submit your answer to jmj0313@kaist.ac.kr **before 11:45 AM**.
- ❖ You can write your answers on any blank A4 sheet of paper.
 - ✓ Write your name/ID in each sheet
- ❖ If you have any questions, raise your hand.
- ❖ You must show all work.
 - ✓ Solutions without supportive work may not receive full credit.

Use complementary input or output variables (e.g. A' , f') where necessary, unless otherwise specified.

Simplify the equations and logic diagrams for full credit, unless otherwise specified.

Use the minimum number of gates for full credit, unless otherwise specified.

1. [Total 80 Pts.] Variants of the problems provided in the course materials.

(a) [10 Pts.] Add $11 + (-31)$ in binary, using the 2's complements to represent negative numbers and a word length of 7 bits (including sign). Discuss whether the 7-bit result is correct.

(b) [20 Pts.] Derive the most simplified expression in (i) sum-of-products and (ii) product-of-sums forms with the Karnaugh map below.

		cd			
ab		00	01	11	10
	00	0	1	0	0
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	0	1

(c) [20 Pts.] Given: $f(a,b,c,d) = \sum m(0,1,2,4,5,9,11,13,15)$.

Note: Do not use inverters. Use complementary input/output variables (e.g. a' , f') where necessary.

- Implement f using 2-input AND and 2-input OR gates.
- Convert the circuit in (i) to a circuit using only 2-input NOR gates.

(d) [20 Pts.] Consider the block diagrams shown below.

 


Fig. 1A.

 



Fig. 1B

- Implement the 2-to-4 decoder (Fig.1A) using 2-input AND gates and inverters. Give its truth table.
- Implement the 1-to-4 demultiplexer (demux; Fig.1B) using the block diagram for the decoder in Fig. 1A, 2-input AND gates, and new signals where necessary. Give its truth table.

- (e) [10 Pts.] Write the simplified Boolean equations of the circuit whose output (f_1 and f_2) are defined by the following truth table. Note that the output may be undefined for some of the input combinations. Simplify the equations for full credit.

a	b	c	f_1	f_2
0	0	0	1	1
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	1	1	0

 2. [Total 20 Pts.] Convert the circuit shown below to a similar one using only 2-input NAND gates. Do not use inverters. Do not use complementary inputs or outputs.



3. [Total 30 Pts.] Consider the function $F(x,y,z,w) = \sum m(1,4,7,9,14)$ with don't care conditions $d(x,y,z,w) = \sum d(0,3,5,6,12)$. Justify your answers by using Karnaugh maps.
- Find all prime implicants.
 - Find all essential prime implicants.
 - Give the minimal sum of products expression for F .
4. [Total 20 Pts.] Using the Boolean Postulates and Theorems, show that
- $$(c' + abd + b'd + a'b)(c + ab + bd) = d(b + c) + b(a + c)(a' + c')$$

Note: Show each step.

5. [Total 30 Pts.] Students have only one 8-bit adder (Fig. 2A) that takes two 8-bit operands, $A(=a_7a_6a_5a_4a_3a_2a_1a_0)$ and $B(=b_7b_6b_5b_4b_3b_2b_1b_0)$, and produces one 8-bit output, $S(=s_7s_6s_5s_4s_3s_2s_1s_0) = A + B$. You can ignore carry out of $A + B$.

 


Fig. 2A. 8-bit adder

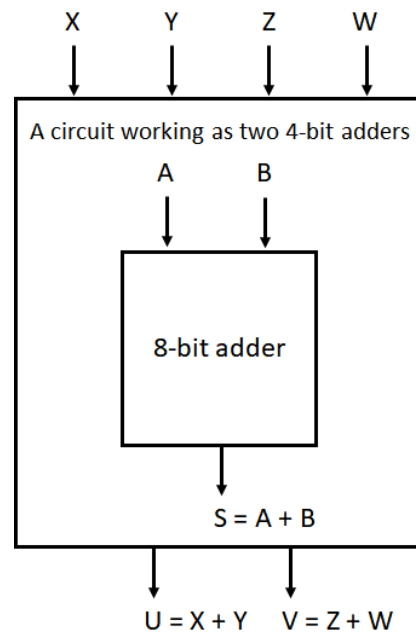


Fig. 2B. Your design

Using the 8-bit adder and other logic gates (e.g. XOR), students need to design a digital circuit that has the same functionality as two 4-bit adders (Fig. 2B). Your design will receive four 4-bit operands, $X(=x_3x_2x_1x_0)$, $Y(=y_3y_2y_1y_0)$, $Z(=z_3z_2z_1z_0)$, and $W(=w_3w_2w_1w_0)$, and must produce two 4-bit outputs, $U(=u_3u_2u_1u_0) = X + Y$ and $V(=v_3v_2v_1v_0) = Z + W$. You can ignore carry out of $X + Y$ and $Z + W$.

Design the circuit by defining Boolean expressions of each bit of A, B, U, and V in terms of X, Y, Z, W, S, and logic 0 or 1 level (e.g. $v_2 = s_2$, $a_3 = 0$).

Note: There may be many different solutions. Use one 8-bit adder and other logic gates. Keep your design simple for full credit.