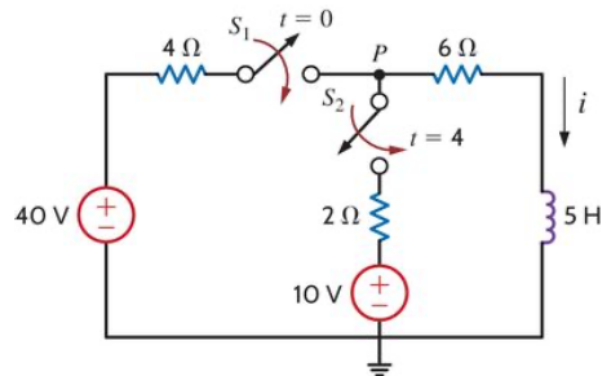


1. (6 Points) At $t = 0$, switch 1 is closed as shown, and switch 2 is closed 4-second later. Find $i(t)$ for $t > 0$.



For $t < 0$, switches S_1 and S_2 are open so that $i = 0$. Since the inductor current cannot change instantly,

$$i(0^-) = i(0) = i(0^+) = 0$$

For $0 \leq t \leq 4s$, S_1 is closed so that the 4-Ω and 6-Ω resistors are in series. Hence, assuming for now that S_1 is closed forever,

$$i(\infty) = \frac{40}{4+6} = 4 \text{ A}, \quad R_{Th} = 4 + 6 = 10 \Omega$$

Thus, $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}} = 4(1 - e^{-2t}) \text{ A}, \quad 0 \leq t \leq 4s$

$i(\infty)$ +1pt

τ +1pt

$i(t)$ +1pt

For $t \geq 4s$, S_2 is closed; the 10-V voltage source is connected, and the circuit changes. This sudden change does not affect the inductor current because the current cannot change abruptly. Thus, the initial current is,

$$i(4) = i(4^-) = 4(1 - e^{-8}) \approx 4 \text{ A}$$

To find $i(\infty)$, let v be the voltage at node P. Using KCL,

$$\frac{40-v}{4} + \frac{10-v}{2} = \frac{v}{6} \quad \Rightarrow \quad v = \frac{180}{11} \text{ V}$$

$$i(\infty) = \frac{v}{6} = 2.727 \text{ A}$$

The Thevenin resistance at the inductor terminals is

$$R_{Th} = 4 \parallel (2 + 6) = \frac{22}{3} \Omega$$

And $\tau = \frac{L}{R_{Th}} = \frac{15}{22} \text{ s}$

Hence,

$$i(t) = i(\infty) + [i(4) - i(\infty)]e^{-\frac{t-4}{\tau}}, \quad t \geq 4$$


$$= 2.727 + 1.273 e^{-1.467(t-4)}, \quad t \geq 4$$

$i(\infty)$ +1pt

τ +1pt

$i(t)$ +1pt

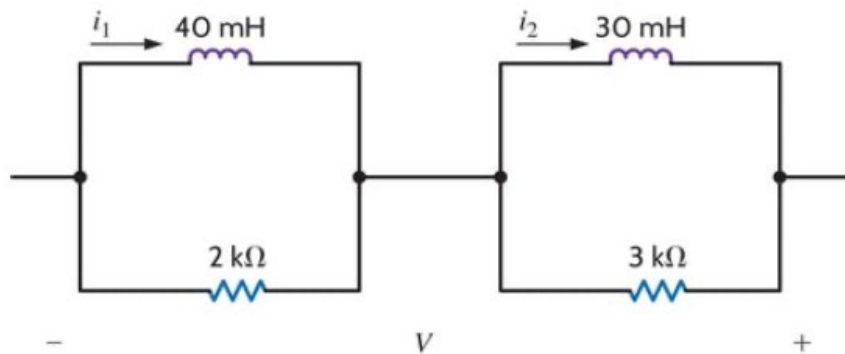2. (6 Points) In the network shown below, initial values are $i_1(0) = 20\text{mA}$ and $i_2(0) = 15\text{mA}$. Determine (a) $V(0)$, (b) $V(t = 15\mu\text{s})$, and (c) the time t when $V(t) = 0.1 V(0)$.



By KVL,

$$40\text{m} \cdot \frac{di_1}{dt} + 2\text{k} \cdot i_1 = 0$$

$$30\text{m} \cdot \frac{di_2}{dt} + 3\text{k} \cdot i_2 = 0$$

, [+1 Points]

and can be expressed

$$\frac{di_1}{dt} + 50\text{k} \cdot i_1 = 0$$

$$\frac{di_2}{dt} + 100\text{k} \cdot i_2 = 0$$

Therefore,

$$i_1 = 20\text{m} \cdot \exp(-50\text{k} \cdot t)$$

$$i_2 = 15\text{m} \cdot \exp(-100\text{k} \cdot t)$$

$$\therefore V(t) = 2\text{k} \cdot i_1 + 3\text{k} \cdot i_2 = 40 \cdot \exp(-50\text{k} \cdot t) + 45 \cdot \exp(-100\text{k} \cdot t) \quad [+1 \text{ Points}]$$

(a) $V(0) = 85\text{V} \quad [+1 \text{ Points}]$

(b) $V(t = 15\mu\text{s}) = 28.94\text{V} \quad [+1 \text{ Points}]$

(c) [+2 Points]

$$s = \exp(-50\text{k} \cdot t)$$


$$40s + 45s^2 = 0.1 \times 85$$

$$s = 0.1772 = \exp(-50\text{k} \cdot t)$$

$$\therefore t = 34.60\mu\text{s}$$

3.

i) $t = 0$.


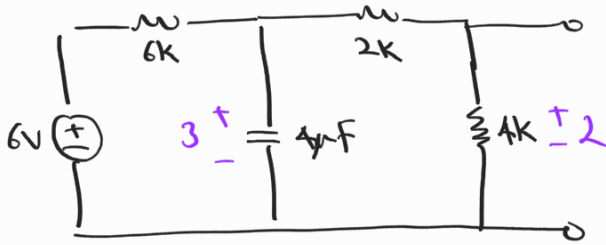


$$V_o(t) \big|_{t=0} = 6 \times \frac{4k}{6k + 2k + 4k}$$

$$= 2 \text{ (V)}$$

initial value of $V_o(t)$... 2 points

ii) $t > 0$

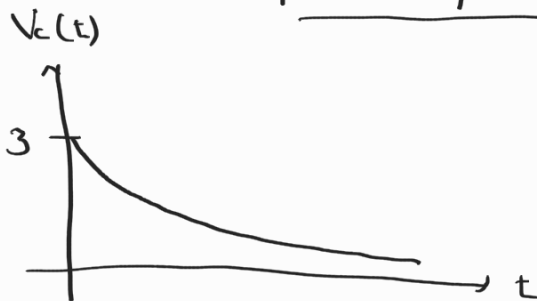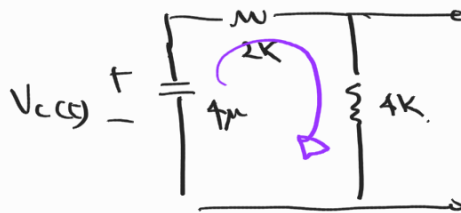

$$\tau = RC$$

$$= 6k \cdot 4\mu$$

$$= 24 \text{ ms}$$

$$V_c(t) = 3 e^{-t/\tau}$$

$$V_o(t) = V_c(t) \times \frac{4k}{2k + 4k}$$

$$= 2 \cdot e^{-t/\tau}$$

exponential decay & reason
... 2 points

right answer
... 2 points

4. (6 Points) If $R = 20 \Omega$, $L = 0.6 \text{ H}$, what values of C will make a series RLC circuit : (a) overdamped, (b) critically damped, and (c) underdamped?

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Here, $w_0 = \frac{1}{\sqrt{LC}}$, $2\xi w_0 = \frac{R}{L}$, $\xi = \frac{R\sqrt{LC}}{2L} = \frac{R}{2} \sqrt{\frac{C}{L}}$

+2 points

Damping factor: $\frac{R}{2} \sqrt{\frac{C}{L}}$

Use equation +1 points

- 1) Damping factor > 1 (Overdamped), $= 1$ (Critically damped), < 1 (Underdamped)
- 2) Discriminant $\left(\left(\frac{R}{L}\right)^2 - 4\frac{1}{LC}\right)$
 > 0 (Overdamped), $= 0$ (Critically damped), < 0 (Underdamped)

(a) Overdamped: $C > \frac{4L}{R^2} = 4 \times \frac{0.6}{400} = 6 \times 10^{-3} \text{ F}$, or $C > 6\text{mF}$ +1 points

(b) Critically damped: $C = \frac{4L}{R^2} = 6\text{mF}$ +1 points


(c) Underdamped: $C < \frac{4L}{R^2} = 6\text{mF}$ +1 points

If condition of damping factor (Discriminant) is correct, but incorrect equation → Total 3 points, (If condition is also incorrect → 2points)

Any calculation error in (a), (b), (c): -1 points

No unit (or wrong unit): -0.5 points

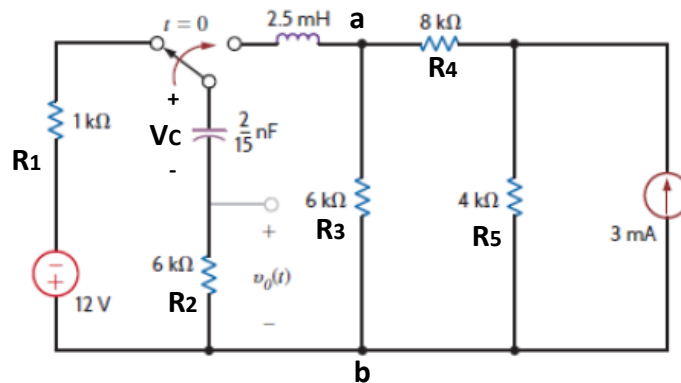5. (6 points) Find $V_o(t)$ for $t > 0$ in the circuit and plot the response including the time interval just prior to moving the switch



i) $t = 0^-$:


$$V_C(0^-) = -12 \text{ [V]}, V_O(0^-) = 0 \text{ [V]}, I_L(0^-) = 0 \text{ [A]}$$

... 0.5pts

$$V_{ab, \text{opencircuit}} = \left(\frac{R_3}{R_3 + R_4 + R_5} \right) \times 12 \text{ [V]} = 4 \text{ [V]}$$

... 0.5pts

ii) $t > 0$:

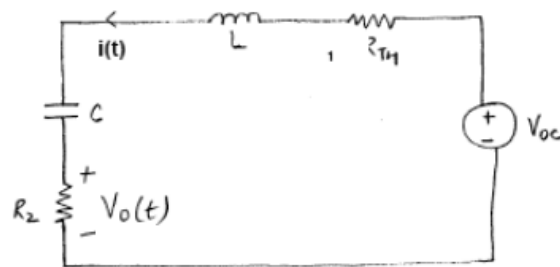

$$R_{TH} = (R_4 + R_5) || R_3 = 4 \text{ k}\Omega$$

$$(R_2 + R_{TH}) \cdot i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = V_{OC}$$

$$\frac{d^2 i(t)}{dt^2} + \frac{R_2 + R_{TH}}{L} \frac{di(t)}{dt} + \frac{i(t)}{LC} = 0$$

$$\lambda = \frac{-4 \times 10^6 \pm \sqrt{(4 \times 10^6)^2 - 4 \cdot (1) \cdot (3 \times 10^{12})}}{2} = -2 \times 10^6 \pm 1 \times 10^6$$

... 0.5pts

\therefore The given situation is an overdamped case :

$$i(t) = K_1 e^{\lambda_1 t} + K_2 e^{\lambda_2 t}$$

$$\rightarrow i(t) = K_1 e^{-1 \times 10^6 t} + K_2 e^{-3 \times 10^6 t}$$

... 0.5pts

$$\rightarrow \frac{di(t)}{dt} = -1 \times 10^6 \times K_1 e^{-1 \times 10^6 t} - 3 \times 10^6 \times K_2 e^{-3 \times 10^6 t}$$

utilizing KVL, we obtain

$$V_{OC} = (R_{TH} + R_2)i(t) + L \frac{di(t)}{dt} + V_C(t)$$

$$\frac{di(t)}{dt} = \frac{V_{OC}}{L} - \frac{R_{TH}+R_2}{L}i(t) - \frac{1}{L}V_C(t) = \frac{4}{2.5m} - \frac{(4k+6k)}{2.5m}(0) - \frac{1}{2.5m}(-12)$$

$$\frac{di(t)}{dt} \Big|_{t=0} = 6400 = -1 \times 10^6 K_1 - 3 \times 10^6 K_2$$

... 0.5pts

$$i(0) = i_L(0^+) = i_L(0^-) = 0 [A]$$

... 0.5pts

$$K_1 + K_2 = 0$$

$$K_1 = 0.0032, K_2 = -0.0032$$

... 1pts


$$i(t) = 3.2e^{-1 \times 10^6 t} - 3.2e^{-3 \times 10^6 t} [mA], t > 0$$

$$v_O(t) = i(t)R_2 = 19.2e^{-1 \times 10^6 t} - 19.2e^{-3 \times 10^6 t} [V], t > 0$$

... 0.5pts

$$= 0[V], t < 0$$

... 0.5pts

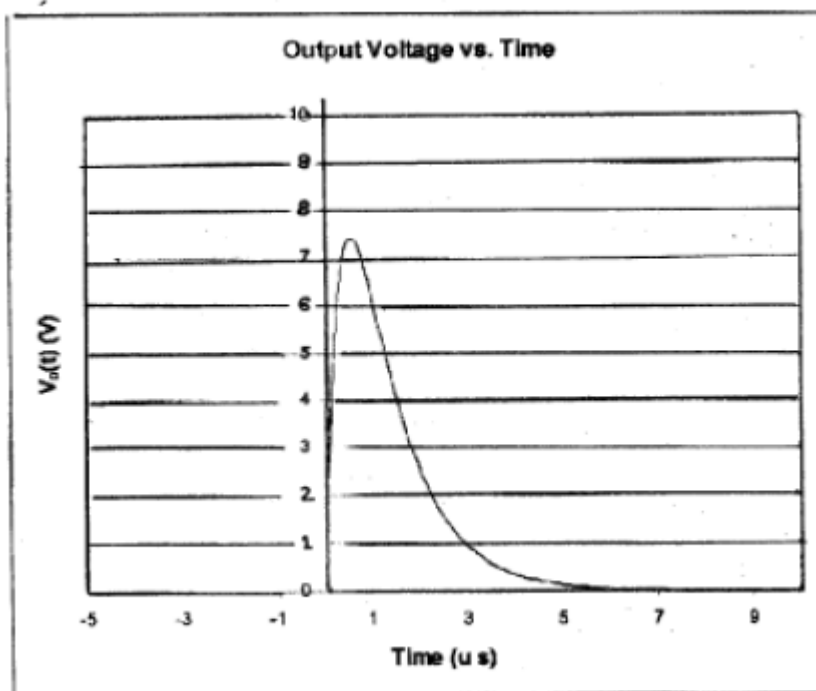

... 1pts