

1

CD \ AB	00	01	11	10
00	0	1	1	1
01	1	0	1	1
11	1	1	0	1
10	1	1	1	0

In min. SOP, $f = AC' + BD' + A'C + B'D$

In min. POS, $f = (A+B+C+D)(A+B'+C+D')(A'+B+C'+D)(A'+B'+C'+D')$

Partial score: X

2


a. +5pts

A	B	Q	Q+
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$Q^+ = AB + QA + QB$$

Partial score: correct state table (+2pts), correct characteristic equation (+3pts)

b. +10pts

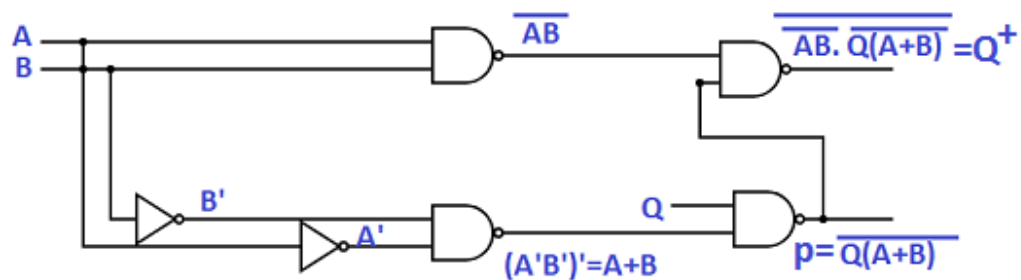

Partial score: correct functionality, but wrong component (-2pt for each component)


3.

Clock cycle	Input Data	EnIn	EnAd	LdAc	LdAd	Accumulator Register	Addend Register	Bus
0	18	1	0	1	0	0	0	18
1	13	1	0	0	1	18	0	13
2	15	0	1	1	0	18	13	31
3	93	1	0	0	1	31	13	93
4	47	0	1	1	0	93	93	124
5	22	1	0	0	1	124	93	22
6	0	0	1	0	0	124	22	146

정답시 10점

정답이 아닐 경우: 칸 18개중 1개 맞을 때 마다 0.5점

4.

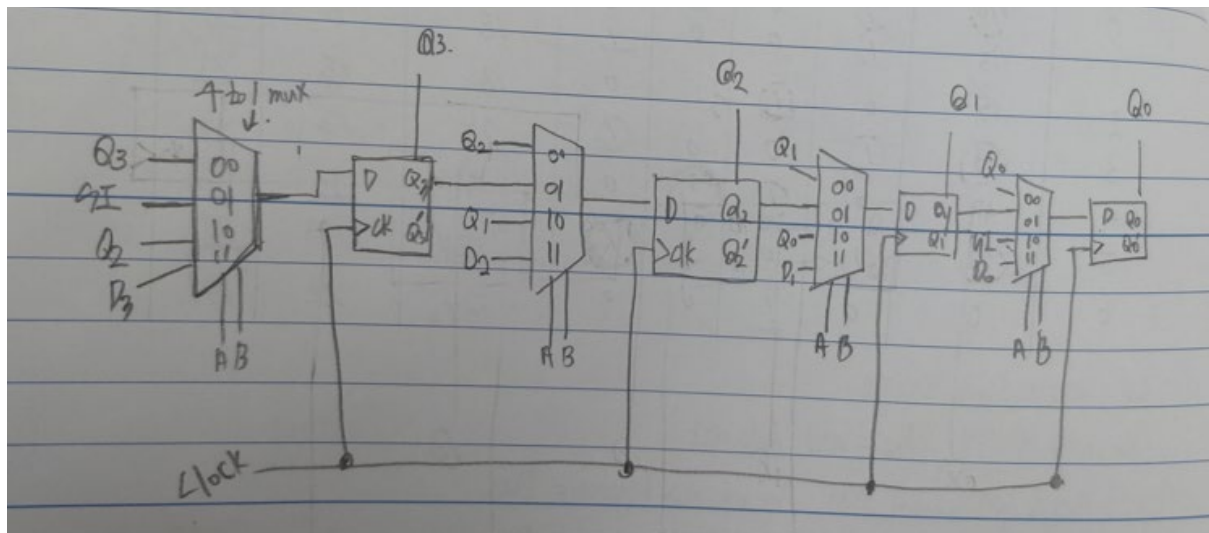

정답시 15점

정답이 아닐 경우:

정답 회로에서 SI 표기를 안하면 -5점

Load 기능 구현시: +4점

Right shift 구현시: +4점


Left shift 구현시: +4점

5. A sequential circuit with one input and one output is used to stretch the first two bits of a 4-bit sequence as follows:

Input	Output
00XX	0000
01XX	0011
10XX	1100
11XX	1111

After every 4 bits, the circuit resets. Find a Mealy state transition graph (minimum number of states) and state table for the circuit. [10 pts]

Sol)

 

→ 5 pts

State	Next State		y/z	
			x	
	x=0	x=1	x=0	x=1
S ₀	S ₁	S ₅	0	1
S ₁	S ₂	S ₃	0	0
S ₂	S ₄	S ₄	0	0
S ₃	S ₆	S ₆	1	1
S ₄	S ₀	S ₀	0	0
S ₅	S ₂	S ₃	1	1
S ₆	S ₀	S ₀	1	1

→ 5 pts

Minimum #states 로 구현하지 않았지만 기능이 맞은 경우 → 2 pts

6. A sequential circuit contains two D flip-flops; their input expressions are $D_1 = XQ_1 + XQ_2$ and $D_2 = XQ_1 + XQ_2'$, where X is a circuit input. Convert the circuit into an equivalent one where each D flip-flop is replaced by a T flip-flop. Derive new flip-flop input expressions.

DFF to TFF transfer: $T = DQ' + D'Q$

D	Q_n	Q_{n+1}	T
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

- $T_1 = D_1Q_1' + D_1'Q_1 = (XQ_1 + XQ_2)Q_1' + (XQ_1 + XQ_2)'Q_1 = XQ_1'Q_2 + X'Q_1$ [5pts]
 → $T_2 = D_2Q_2' + D_2'Q_2 = (XQ_1 + XQ_2')Q_2' + (XQ_1 + XQ_2')'Q_2 = XQ_2' + X'Q_2 + Q_1'Q_2$ [5pts]

Boolean expression expanding mistake -2pts

7. The following are possible state assignments for a six-state sequential circuits.

	(i)	(ii)	(iii)	(iv)	(v)
S_0	000	010	100	110	001
S_1	001	111	101	010	111
S_2	010	001	000	111	101
S_3	011	110	001	011	011
S_4	100	000	111	000	000
S_5	101	100	110	100	010

- a. Which two state assignments are equivalent?

Complement of (iv) and swap first and last column → (iii)
 (iii) and (iv) are equivalent [5pts]

- b. For each assignment (except (i)), give an equivalent assignment for which state S_0 is assigned to 000.

	(ii)	(iii)	(iv)	(v)
S_0	000	000	000	000
S_1	101	001	100	110
S_2	011	100	001	100
S_3	100	101	101	010
S_4	010	011	110	001
S_5	110	010	010	011

[10 pts] each assignment 2.5pts

If (iv) and (iii) represent the same, it is also answer

8. Make a circuit which gives the absolute value of a 4-bit 2's complement number. Use full adders, multiplexers, and inverters.

For 4-bit binary number $X = X_3X_2X_1X_0$

If $X > 0$: $|X| = X$

If $X < 0$: $|X| = -X$


2's complement is calculated like below

2's complement of $X_3X_2X_1X_0 = X_3'X_2'X_1'X_0' + 0001$

Output $Y = Y_3Y_2Y_1Y_0$ which is $|X|$

So if X is positive number ($X_3 = 0$), $Y = X_3X_2X_1X_0$,

 If X is negative number ($X_3 = 1$), $Y = 2$'s complement of $X_3X_2X_1X_0$



If circuit is functionally well, answer is correct [15 pts]

Only functional for 1 condition (positive/negative) [5pts]